

JOIN **PUNE ENGINEERS** **PUNE ENGINEERS** **WHATSAPP CHANNEL**

All Subject Notes:

<https://www.studymedia.in/fe/notes>



JOIN COMMUNITY OF 30K+ ENGINEERS

CLICK HERE TO JOIN



SCAN ME



UNIT - II

Transistor and OPAMP

- * Bipolar Junction Transistor :-
 - After diode, the next invention in the semiconductor devices is a Bipolar Junction Transistor.
 - Transistor is a three terminal device : Base, emitter, collector.
 - It can be operated in three configurations common base, common emitter and common collector.
 - According to configuration it can be used for voltage as well as current amplification.

* Advantages of Transistor :-

- very small size and weight, reducing equipment size.
- low operating voltages.
- lower costs.
- low power consumption.
- Higher efficiency.
- Very low sensitivity to mechanical shock or vibration.
- very long life.

* Types of Transistor.


- Unipolar Junction Transistor (UJT)
- Bipolar Junction Transistor (BJT)

- In UJT, the current conduction is only due to one type to one type of charge carriers, majority carriers.
e.g. FET


- The current conduction in BJT is be of both types of charge carriers, holes and electrons.
It is current controlled or current operating device.

* Types of BJT


1) n-p-n

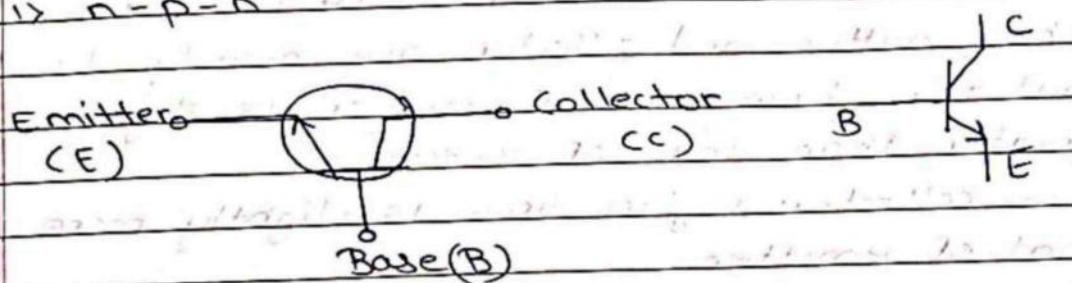

2) p-n-p

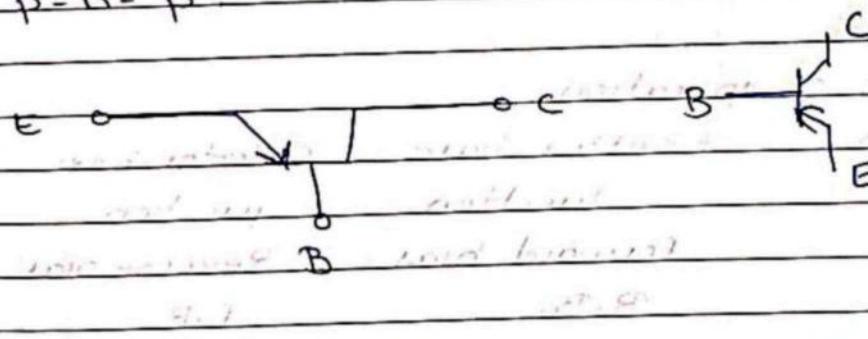

* Construction of BJT

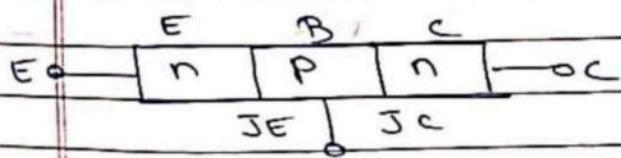

single p region is sandwiching between two n region.

Fig. a) n-p-n

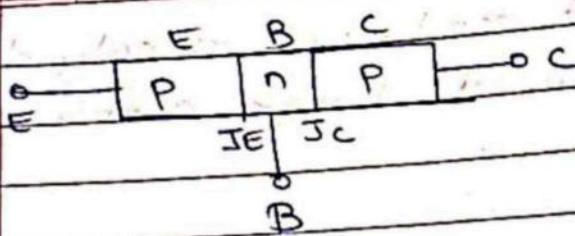


Fig. b > p-n-p

- The middle region of each transistor type is called base of the transistor. This region is very thin and lightly doped.

- The process by which impurities are added to a pure semiconductor is called doping.

- The emitter and collector are heavily doped. But the doping level in emitter is slightly greater than that of collector.

- The collector region-area is slightly more than that of emitter.

- A transistor has two p-n-junctions.

a) Emitter Junction (JE)

b) Collector Junction (JC)


* Regions of operation

Region	Emitter-base junction	Collector-base junction	Application
--------	-----------------------	-------------------------	-------------


1. Active	Forward bias	Reverse bias	Amplification
2. Cut-off	R.B.	F.B.	OFF State
3. Saturation	F.B.	R.B.	ON State
4. Inverse active	R.B.	F.B.	-

In order to operate transistor as an amplifier it is necessary to bias it in the active region.

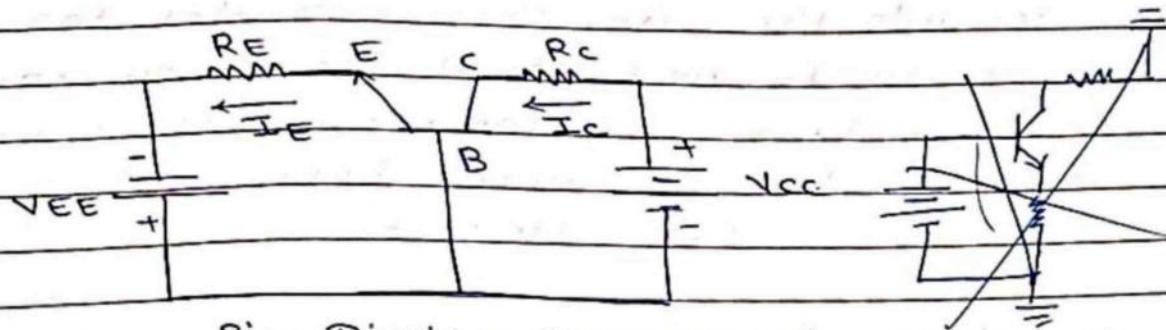- * Working of npn and pnp Transistors.
- * Working of npn Transistor.



Pig. Biasing arrangement.

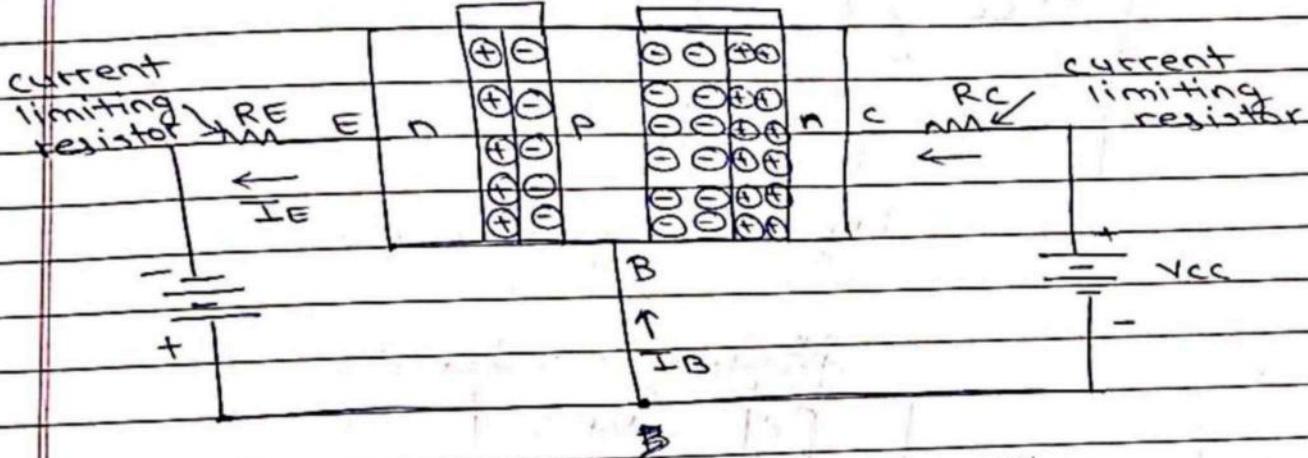


Pig. Operation of npn transistor in active region.

- The supply voltage VEE , forward biases the emitter junction (JE) and the supply voltage V_{CE} reverse biases the collector junction (J_C)
- The base to emitter junction is forward biased by the d.c. source VEE . Thus, the width of depletion region at this junction is small.
- The collector to base junction is reverse biased and hence width of depletion region at this junction is large.


- The forward biased EB junction causes the electrons in the n-type emitter to flow towards the base. This constitutes the emitter current I_E . As these electrons flow through the p-type base, they tend to combine with holes in p-region (base).
 $I_E = I_B + I_C$.

* Working of npn Transistor

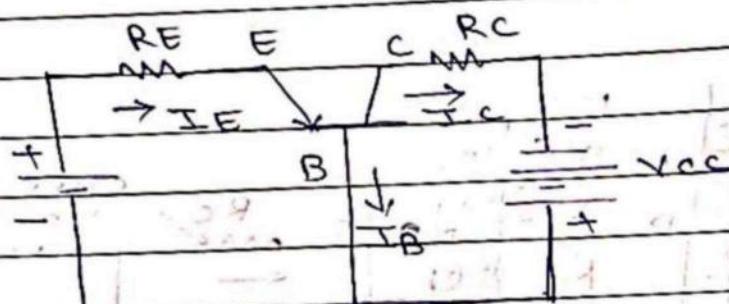

Rig. Biasing arrangement.

BE depletion CB depletion

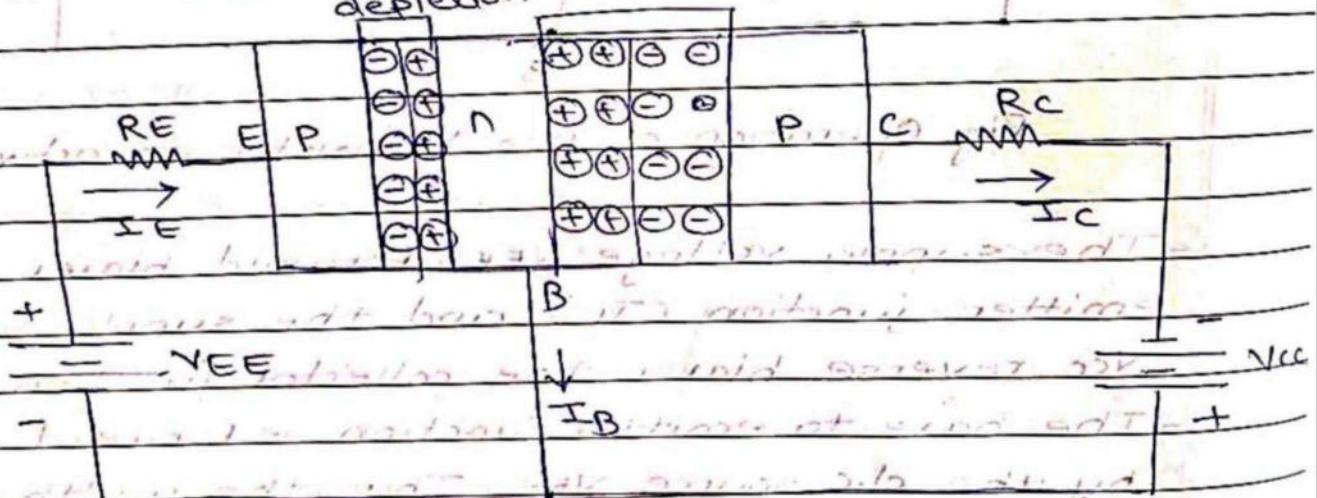


- The forward biased EB junction causes the holes in the p-type emitter to flow towards the base. This constitutes the emitter current I_E .

- As these holes flow through the n-type base, they tend to combine with electrons in n-region (base).
- As the base is very thin and lightly doped, very few of the holes injected into the base from the emitter recombine with electrons to constitute base current, I_B .
- The remaining large number of holes cross the depletion region and move through the collector region to the negative terminal of the external dc source. This constitutes collector current I_C .
- Forward biased EB junction also causes electrons to flow through from n-type base to p-type emitter. But as base is lightly doped electron becomes the minority carriers. Thus the hole flow constitutes the dominant current in an pnp transistor.
 $I_E = I_B + I_C$.


- * CB, CE, CC configuration and V-I characteristics
- The transistor can be connected in a circuit in the following three configurations:-
 - 1) Common base configuration
 - 2) Common emitter configuration
 - 3) Common collector configuration.

2) Common Emitter Configuration:

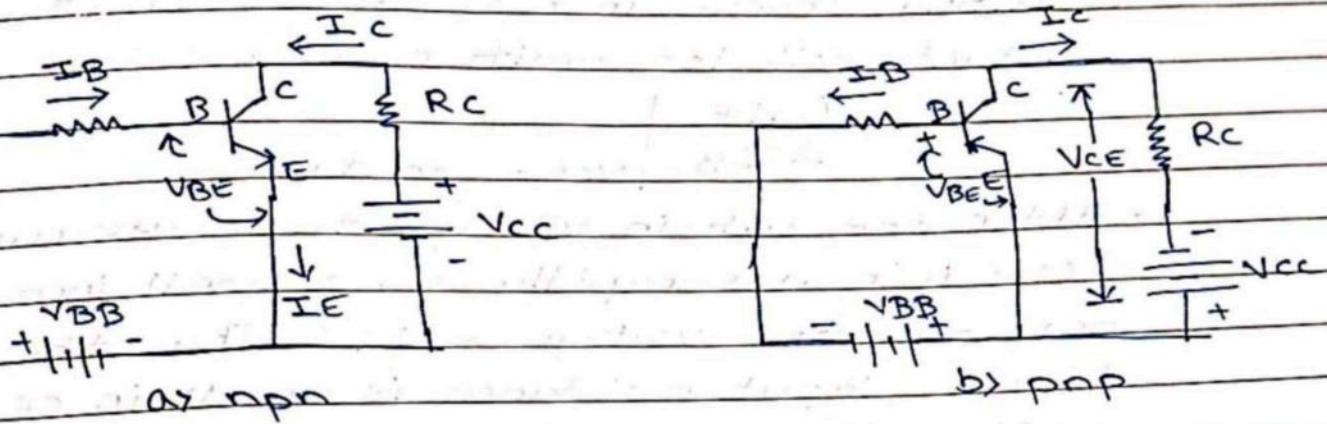

- In this configuration input is applied between base and emitter, and output is taken from collector and emitter.
- Here, emitter of the transistor is common to both, input and output circuits, and hence the name common emitter configuration.

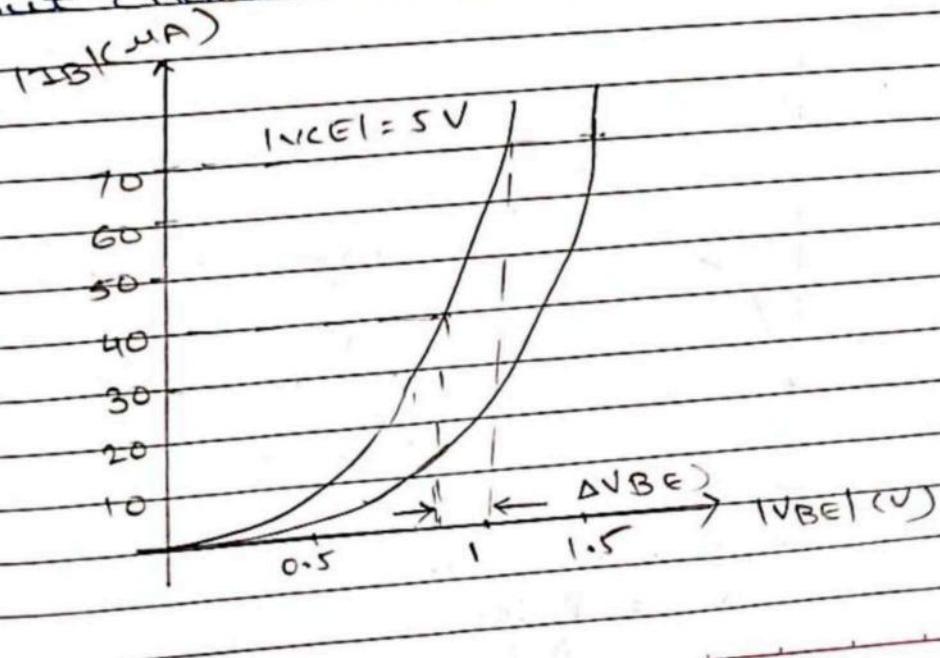Input characteristics of CE Configuration:-



- The input resistance is the ratio of change in base-emitter voltage (ΔV_{BE}) to the resulting change in base current (ΔI_B) at constant collector-emitter voltage V_{CE}


$$r_i = \frac{\Delta V_{BE}}{\Delta I_B}$$

$$\Delta I_B \quad | \quad V_{CE} = \text{constant}$$

- After the cut-in voltage, the base current (I_B) increases rapidly with small increase in base-emitter voltage (V_{BE}). Thus the dynamic input resistance is small in CE configuration.

- For a fixed value of V_{BE} , I_B decreases as V_{CE} is increased.

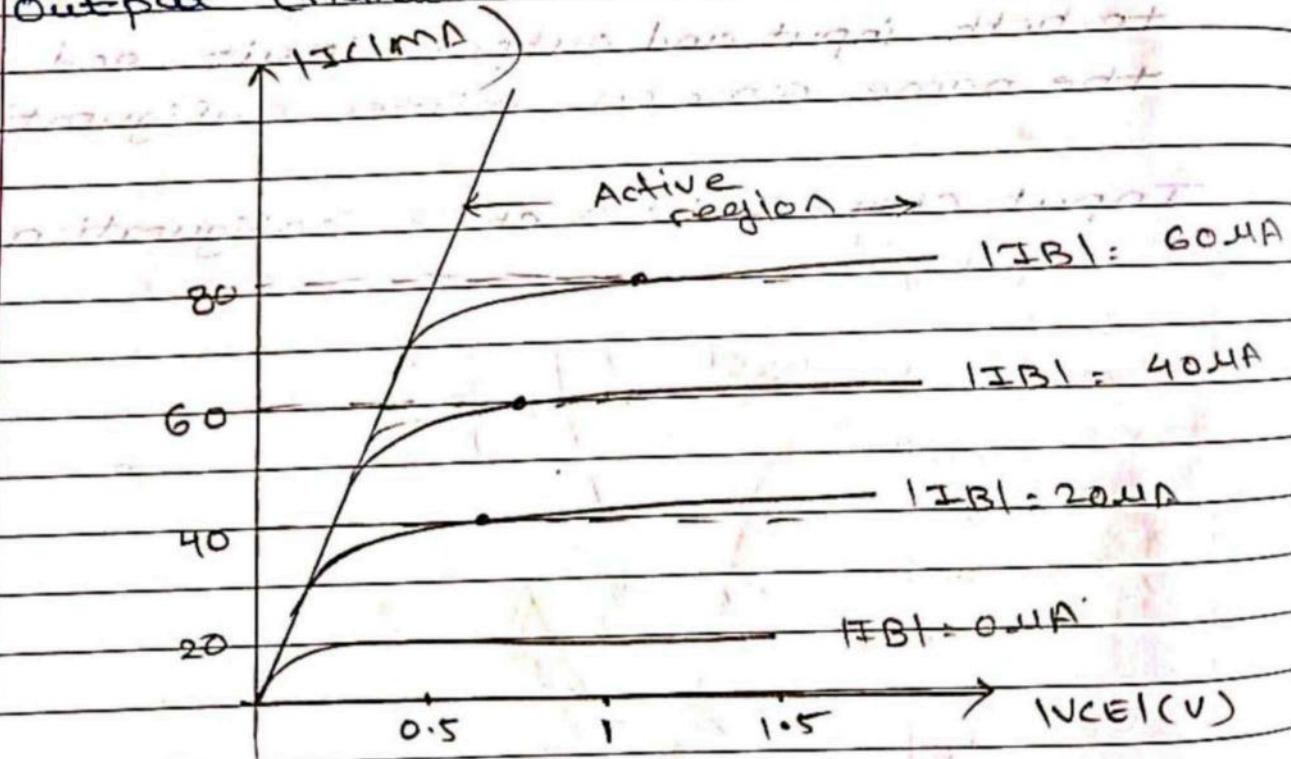Output characteristics of CE configuration:



Q1P Dynamic resistance:-

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}$$

$$\Delta I_C \quad | \quad I_B = \text{constant OR } \Delta I_B = 0$$

a) Active Region:-

- For the operation of active region, JF is in F.B. and I_C is in R.B.

- I_C rises more sharply with increasing V_{CE} in the linear region of output characteristics of CE transistor.

b) Saturation Region:-

- In this region, JF & I_C both are F.B.

- The saturation value of V_{CE} , designated (V_{CECSAT}) usually ranges between 0.1V to 0.3V.

c) Cut-off region:-

- The region below $I_B = 0$ is the cut-off region of operation for the transistor.

- In this region, both junctions are in R.B.

For saturation region:-

$$I_B > I_C$$

$$\beta_{DC}$$

$$\therefore \beta_{DC} = \frac{I_C}{I_B}$$

For cut-off:-

$$I_B = 0$$

For active region:-

$$V_{CE} > V_{CECSAT}$$

1. Alpha (α):

- it is defined as the ratio of the collector current resulting from carrier injection to the total emitter current.

$$\alpha_{dc} = \alpha = \frac{I_{C(INS)}}{I_E} = \frac{I_C}{I_E}$$

Since $I_C \ll I_E$ the value of α_{dc} is always less than unity

$$\alpha = \frac{I_C}{I_E} = \frac{I_E - I_B}{I_E} = 1 - \frac{I_B}{I_E}$$

Since $I_B \ll I_E$,

α is nearly equal to 1.

$$\therefore I_C = \alpha_{dc} I_E + I_{CBO}$$

2. Beta (β)

- It is defined as the ratio of the collector current to the base current.

$$\beta_{dc} = \beta = \frac{I_C}{I_B}$$

$$I_C = \beta_{dc} I_B + (1 + \beta_{dc}) I_{CBO}$$

$$I_C = \beta_{dc} I_B + I_{CEO}$$

3. Relationship between α and β

$$\text{w.k.t. } \beta = \frac{I_C}{I_B}$$

$$\text{we have, } I_E = I_C + I_B$$

$$\text{i.e. } I_B = I_E - I_C$$

$$\beta = \frac{I_C}{I_E - I_C}$$

Dividing N & D of R.H.S. by I_E , we get

$$\beta = \frac{I_C}{I_E}$$

$$\frac{I_E}{I_E} - \frac{I_C}{I_E}$$

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}}$$

$$\text{W.K.t. } \alpha = \frac{I_C}{I_E} \text{ and } I_E = I_B + I_C$$

$$\alpha = \frac{I_C}{I_B + I_C}$$

Dividing N & D of R.H.S. by I_B . We,

$$\alpha = \frac{I_C}{I_B}$$

$$\frac{I_B}{I_B} + \frac{I_C}{I_B} = 1 + \alpha$$

$$\boxed{\alpha = \frac{\beta}{1 + \beta}}$$

e.g. Calculate values of I_C & I_E for BJT with $\alpha_{dc} = 0.98$ and $I_B = 50 \mu A$. Also determine β_{dc} for BJT.

Given,

$$\alpha_{dc} = 0.98$$

$$I_B = 50 \mu A$$

To find : β_{dc} , I_C & I_E

$$\begin{aligned}\beta &= \beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}} = \frac{0.98}{1 - 0.98} = 49\end{aligned}$$

$$I_C = \beta I_B = 49 \times 50 \mu A$$

$$= 2.45 \text{ mA}$$

$$I_E = I_B + I_C$$

$$= 50 \mu A + 2.45 \text{ mA} = 2.5 \text{ mA}$$

4 Gamma (γ)

- The current gain of CC configuration is given by.

$$\gamma = \frac{I_E}{I_B} = \frac{I_B + I_C}{I_B}$$


$$= 1 + \frac{I_C}{I_B}$$

$$= 1 + \beta$$

$$= \frac{1 + \alpha}{1 - \alpha}$$

$$= \frac{1}{1 - \alpha}$$

* BJT as a switch:

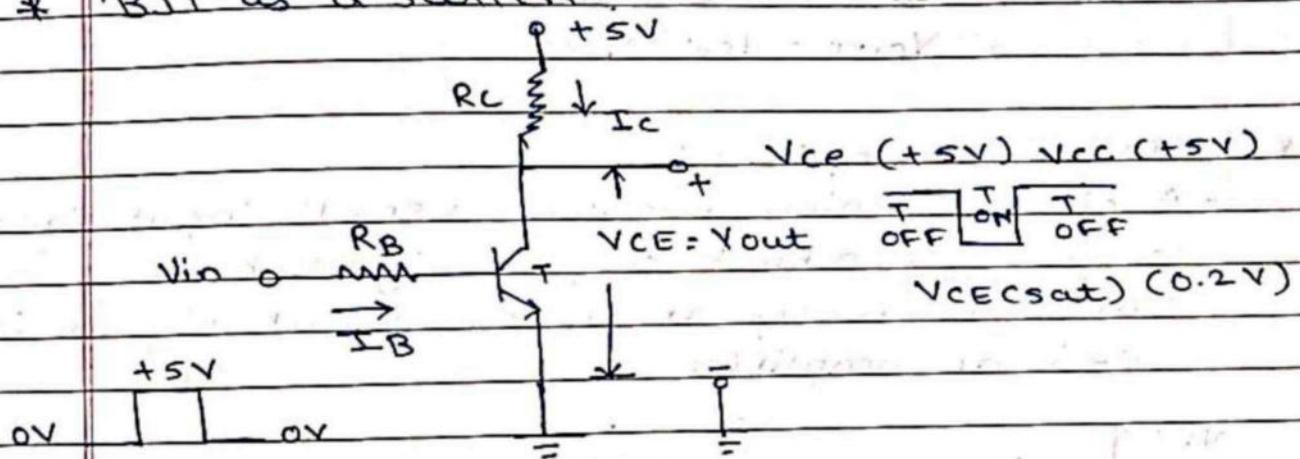

Bjt Transistor as a switch

- In this circuit, when input is HIGH emitter junction is forward biased and base current flows. It is greater than I_C/β , hence transistor is operated in saturation.

- In saturation condition, voltage between collector and emitter, $V_{CE(sat)}$ is typically 0.2V to 0.3V, and hence transistor acts as a closed switch.

- The minimum value of base current needed to operate transistor in saturation is
 $I_{Bmin} = I_{CCsat}$

B

- When input is low, emitter junction and collector junction both are reverse biased and hence transistor is operated in cut-off.
- In cut-off base current is zero and hence collector current is also zero, and transistor acts as an open switch.
- Applying KVL to the collector circuit we have,


$$V_{CC} = I_C R_C + V_{CE}$$

Since $I_C = 0$, we have

$$V_{OUT} = V_{CE} = V_{CC}$$

* BJT as CE Amplifier:-

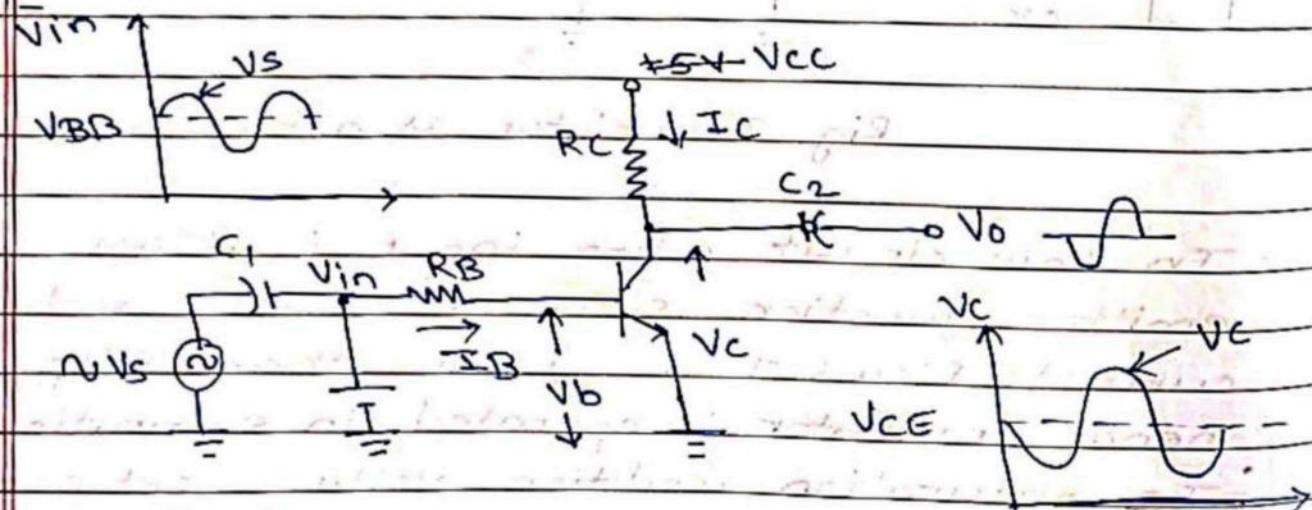- A circuit which amplifies a small input signal to give magnified output signal having same frequency as that of input signal is called an amplifier.



Rig. CE. amplifier circuit

- The ratio of magnitude of output signal to input signal is called the voltage gain of the amplifier.
- It is important to note that the values of R_B and R_C are chosen to operate transistor in active region.
- As shown in Fig a small signal ac voltage, V_S is superimposed on the dc bias voltage V_{BB} by capacitive coupling.
- The small ac input voltage produces an ac base current, which result in a much larger ac collector current.

$$\Delta I_B = \frac{\Delta V_{in}}{R_B}$$

- The corresponding change in collector current, I_C is given by,
- $$\Delta I_C = \beta \Delta I_B = \beta \frac{\Delta V_{in}}{R_B}$$
- The change in the output voltage due to change in the input voltage is given by,

$$\Delta V_o = \Delta I_C R_C$$

$$\therefore \Delta I_C = \beta \frac{\Delta V_{in}}{R_B}$$

$$= \beta \frac{\Delta V_{in} R_C}{R_B}$$

$$= \frac{\beta R_C}{R_B} \Delta V_{in}$$

$$A_V = \frac{\Delta V_o}{\Delta V_{in}} = \frac{\beta R_C}{R_B}$$

- The CE amplifier operated in the active region acts as an voltage amplifier

* Applicability

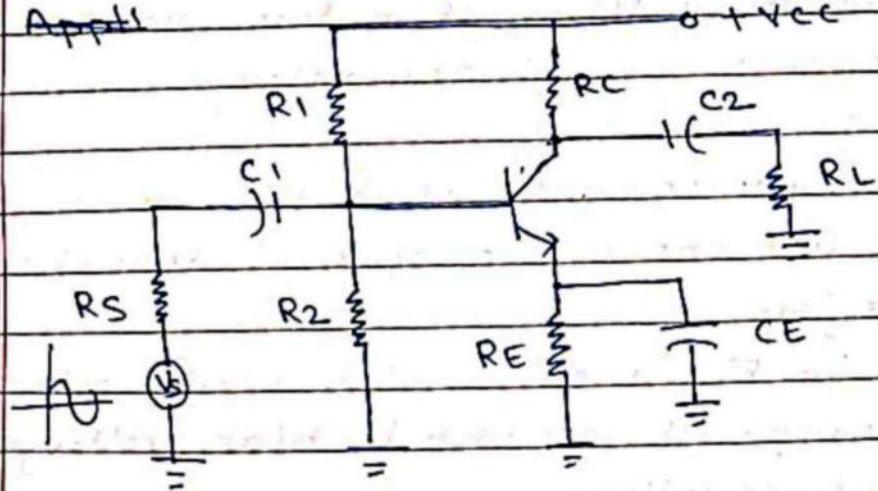


Fig. Practical C.E. amp circuit

- Biasing circuit:-

R_1 , R_2 and R_E forms the voltage divider biasing circuit for CE amplifier. It sets proper operating point for the CE amplifier.

- Input Capacitor C_1 :-

This capacitor couples the signal to the base of the transistor. It blocks any d.c. component present in the signal and passes only a.c. signal for amplification.

- Emitter bypass capacitor C_E :-

C_E is connected in parallel with the R_F , R_E to provide a low reactance path to the amplified a.c. signal.

- Output coupling capacitor C_2 :-

C_2 couples the output of the amplifier to load or to the next stage of amplifier. It blocks d.c. and passes only a.c. part of the amplified signal.

* Applications of BJT :


- Transistor can be used as a switch
- used as an amplifier.
- used as a current and voltage amplifier.
- As a switch. in SMPS and digital circuits.
- used in oscillator circuits and feedback amplifiers

Metal Oxide Semiconductor Field Effect Transistor (MOSFET)

- The MOSFET can be made very small and hence can be used to design high density VLSI circuits.
- The MOSFET differs from the JFET in that it has no p-n junction structure; instead the gate of the MOSFET is insulated from the channel by a silicon dioxide (SiO_2) layer. Due to this the input resistance of MOSFET is greater than JFET. Because of the insulated gate, MOSFETs are also called IGFETs.

* Types of MOSFET

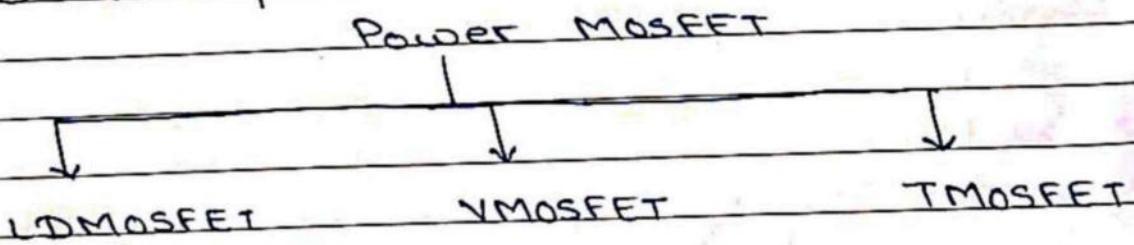- The two basic types of MOSFETs are:
 - a) Depletion (D) MOSFET
 - b) Enhancement (E) MOSFET
- MOSFETs suitable for high power applications are called power MOSFETs.




- MOSFET Designed for RF Amplifications
 - . Dual Gate MOSFET.


Substrate is a foundation layer that supports the transistor structure. Substrate is used to control V_T

PAGE NO.
DATE:

* E-MOSFET :-

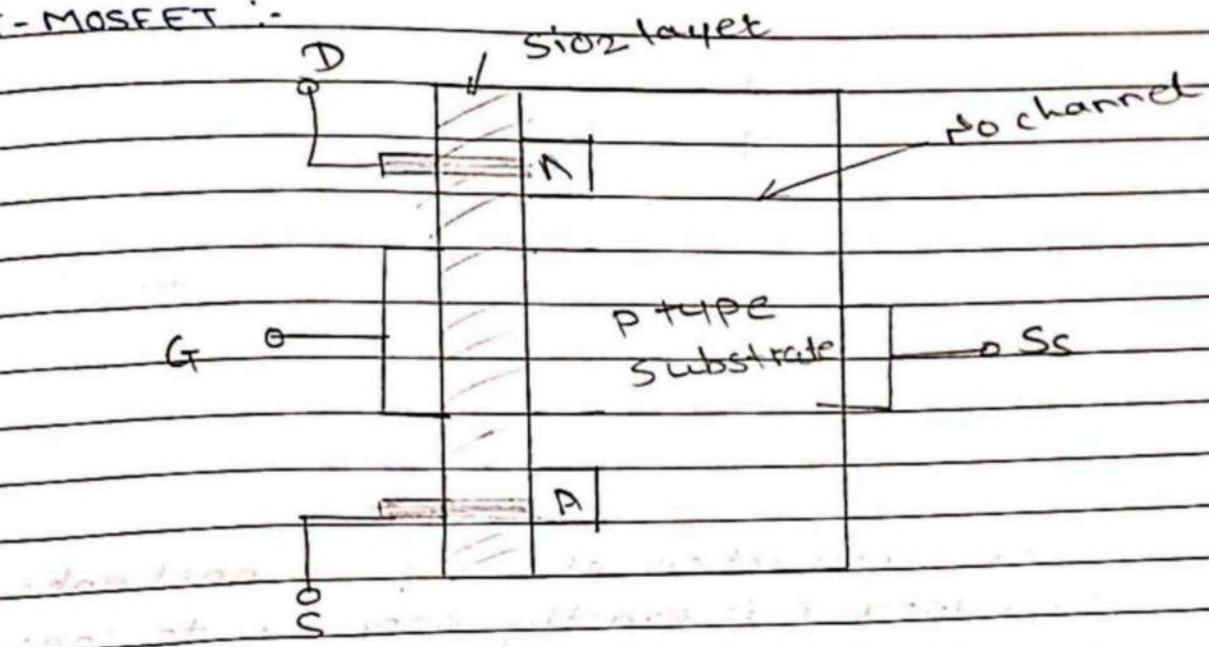


- Fig shows construction of n-channel enhancement type MOSFET
- Two highly doped n-regions are diffused into a lightly doped p-type substrate. The source and drain are taken out through metallic contacts to n-doped regions.
- The channel between two n-regions is absent in the enhancement type MOSFET. The SiO₂ layer is still present to isolate the gate metallic platform from the region between the drain and source, but now it is simply separated from a section of the p-type material.
- It differs in construction from the depletion MOSFET in that it has no physical channel.

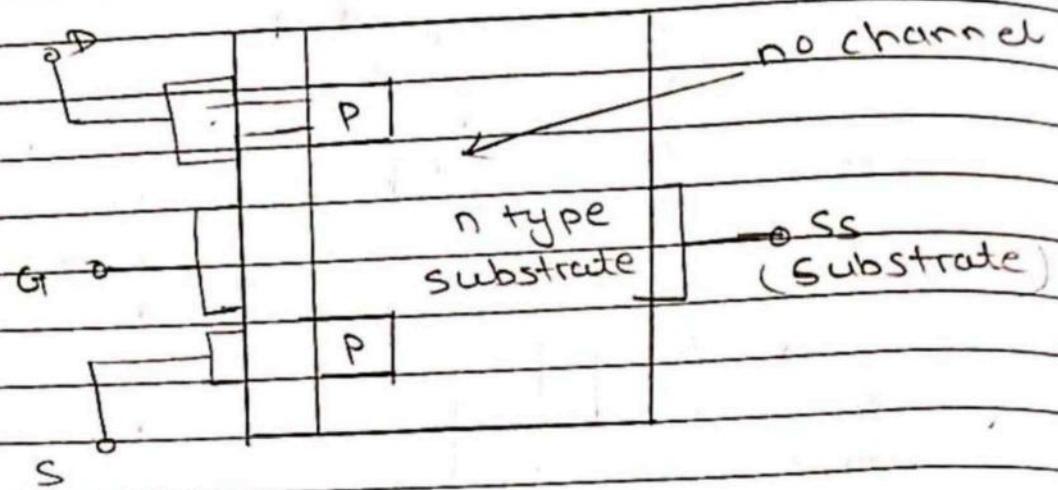

- The construction of the p-channel enhancement type MOSFET is exactly opposite to that of n-channel enhancement type MOSFET.
- Here, the substrate is of n-type and regions are of p-type

* Operation :-

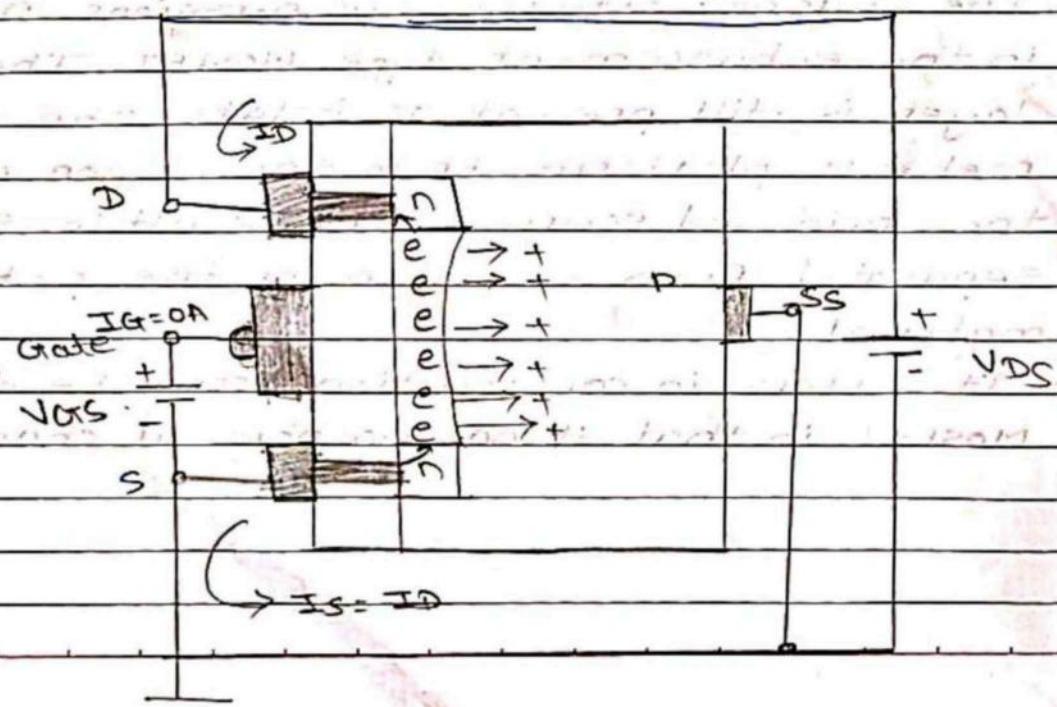- This type of MOSFET operates only in the enhancement mode and has no depletion mode



- $V_{GS} = 0$:

On application of drain to source voltage V_{DS} and keeping gate to source voltage zero by directly connecting gate terminal to the source terminal, practically zero current flows, quite different from the depletion type MOSFET.

- $V_{GS} > 0$:

If we increase magnitude of V_{GS} in the +ve direction, the concentration of electrons near the SiO_2 surface increases. At a particular value of V_{GS} there is a measurable current flow between drain & source.

This minimum value of V_{GS} at which I_D starts flowing is called threshold voltage denoted by V_T .


Thus we can say that in an enhancement type n-channel MOSFET, a positive gate voltage above a threshold value induces a channel and hence the drain current by creating a thin layer of negative charges in the substrate region adjacent to the SiO_2 layer.

$V_{GS} = 0$ - No conduction


$V_{GS} > 0 \dots e^-$ near SiO_2 start to flow current.

- The conductivity of the channel is enhanced by increasing the gate to source voltage thus pulling more electrons into the channel. For any voltage below the threshold value, there is no channel.
- Since the channel does not exist with $V_{GS} = 0$ and is enhanced by the application of a positive gate to source voltage, this type of MOSFET is called an enhancement type MOSFET.

Symbols:- Enhancement MOSFET

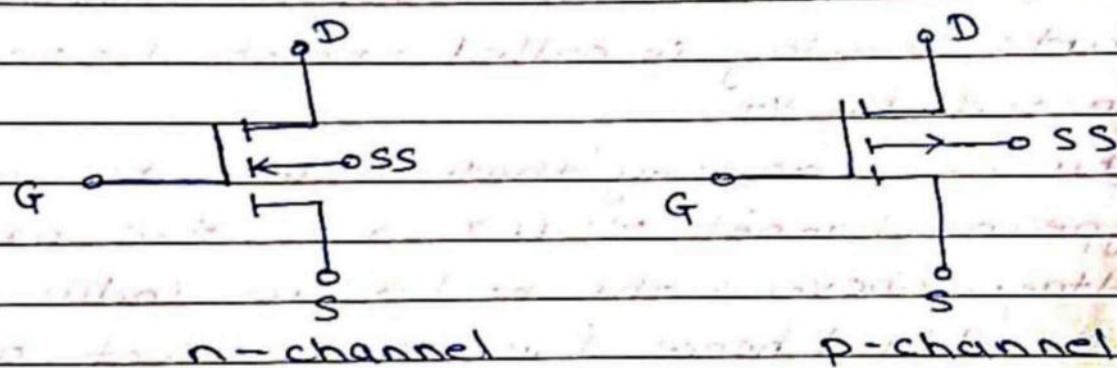

n-channel p-channel

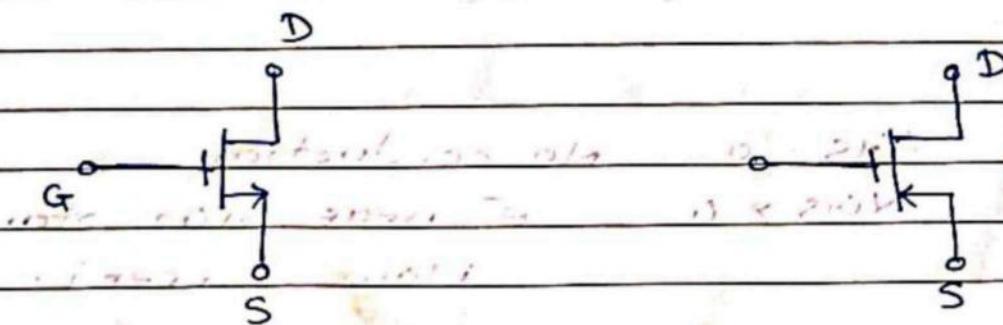


Simplified n-channel

Simplified p-channel

→ characteristics of n-channel FET

a) Transfer characteristics.

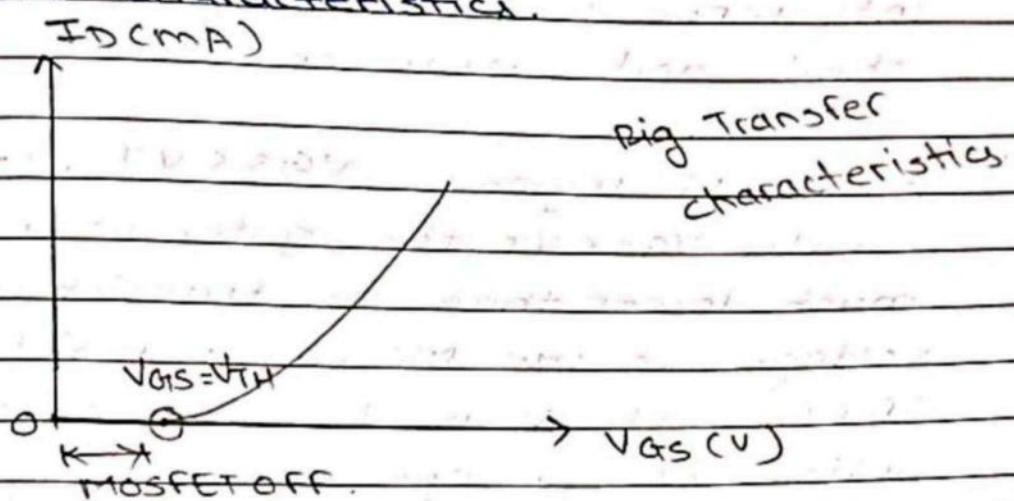


- It is now totally in the positive V_{GS} region and remains zero till $V_{GS} = V_T$ (Threshold voltage)
- The relation betn drain current and V_{GS} is given by.

$$I_D = K (V_{GS} - V_T)^2$$

- This is a non-linear relation and is valid only for $V_{GS} > V_T$. K is constant and its value depends on construction of the device.
- The drain current $I_D = 0$ For $V_{GS} \leq V_T$, whereas I_D increases in an exponential manner with increase in V_{GS} above V_T .

b) Drain characteristics:

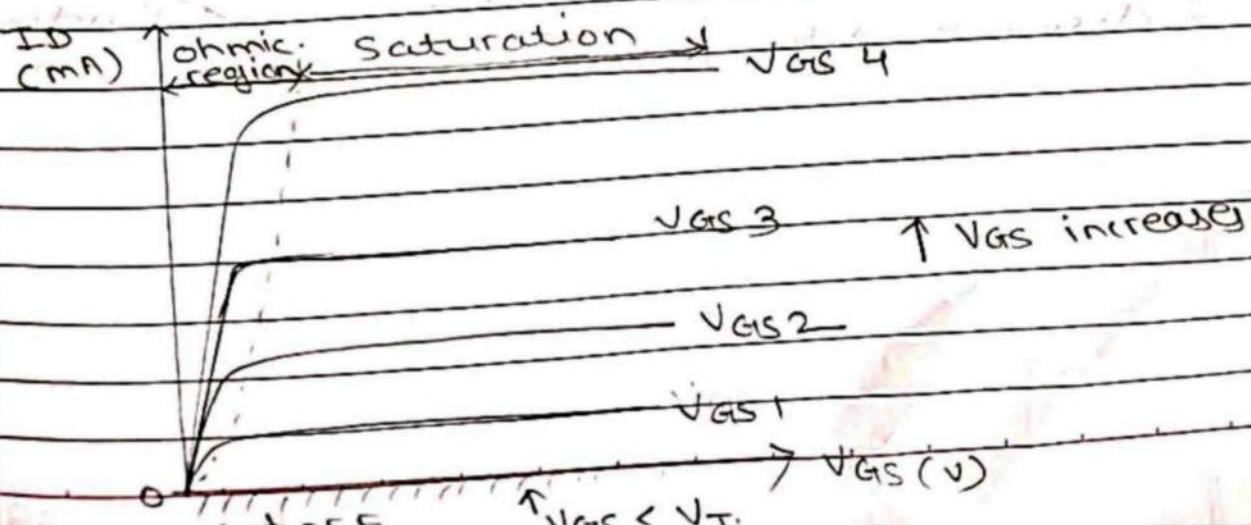


- The drain characteristics has been divided into three regions viz. cut-OFF, linear ohmic and saturation region

i) Cut-OFF region $V_{GS} < V_T$, $I_D = 0$, open switch
with $V_{GS} < V_T$ the gate-source voltage is much lower than the transistors threshold voltage so the MOSFET transistor is switched 'fully-off' thus $I_D = 0$, with the transistor acting like an open switch regardless of the value V_{DS}


ii) Linear (ohmic) Region $V_{GS} > V_T$, $V_{DS} < V_{GS}$
with $V_{GS} > V_T$ & $V_{DS} < V_{GS}$ the transistor is in its constant resistance region behaving as a voltage controlled resistance whose resistive value is determined by the gate voltage, V_{GS} level.

iii) Saturation Region : - closed switch
with $V_{GS} > V_T$ & $V_{DS} > V_{GS}$ the transistor is in its constant current region and is therefore 'Fully-on'. The drain current $I_D = \text{maximum}$ with the transistor acting as a closed switch.

* P-channel E-MOSFET

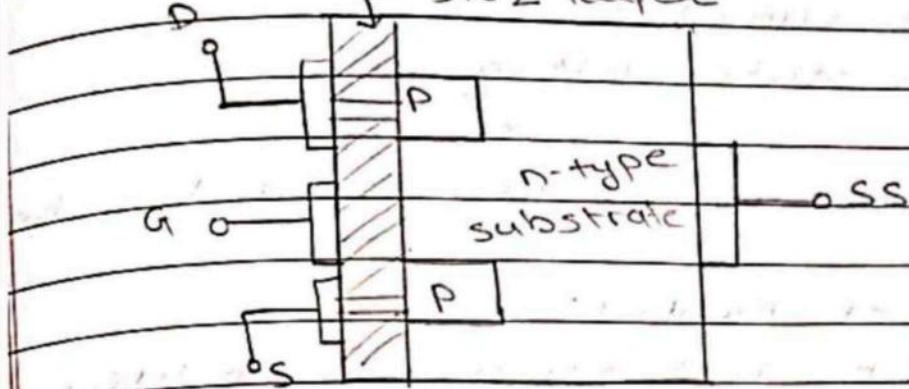


$I_{D(CMA)}$

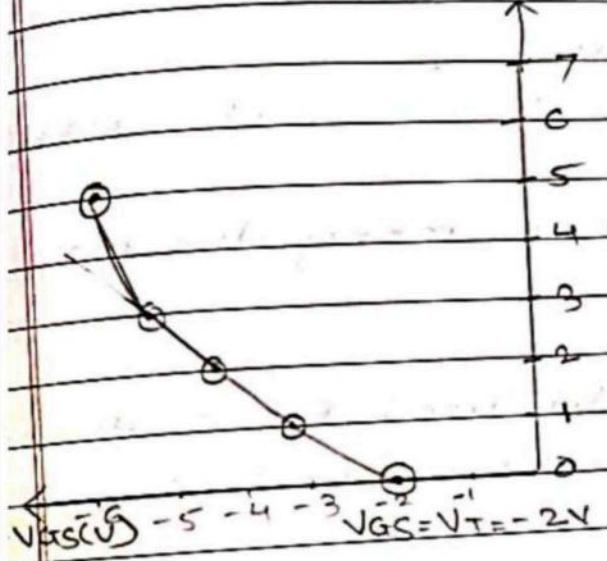

Transfer ch's

$|I_D|(\text{mA})$

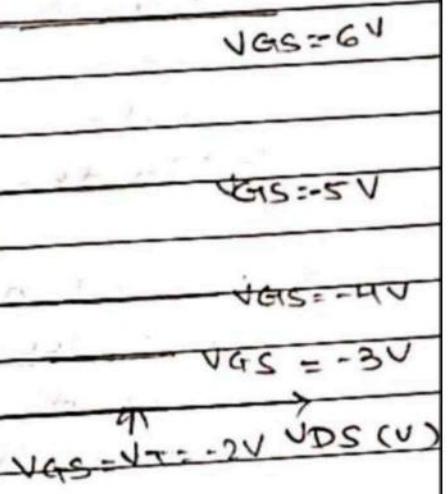

Drain characteristic

Advantages of MOSFET :-

- Very high input resistance (Few G Ω)
- Very low gate current is required.
- Better thermal stability
- Small size
- can operate at a very high frequencies
- low internal noise.

Disadvantages of MOSFET :-


- High input capacitance
- Large on state voltage drop.
- More power loss in the device.
- Handling precautions are required to be followed.

Applications of MOSFET:-


- As a switch, high frequency amplifier.
- As a voltage variable resistance.
- Constant current source.
- In the logic circuits such as inverter, NAND gate.
- In the semiconductor memory devices.

* MOSFET as a switch:-

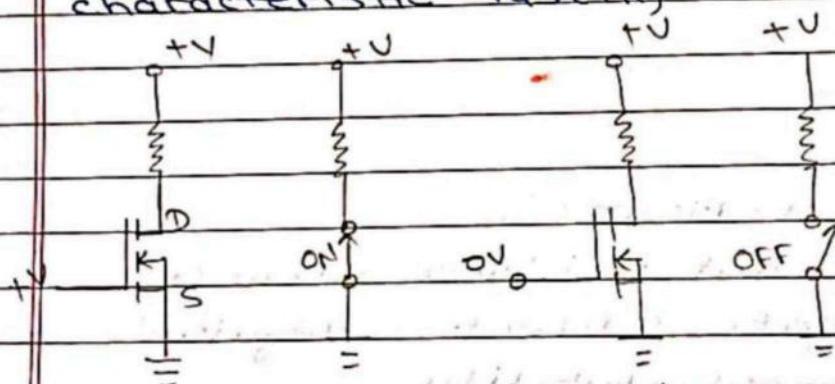- E-MOSFET are generally used for switching applications because of their threshold characteristic $V_{GS(TH)}$



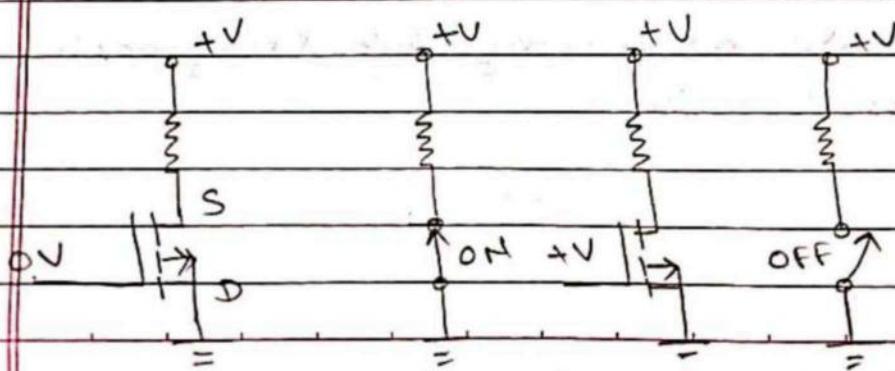Rig. n channel MOSFET & switch equivalent




Rig. p channel MOSFET & switch equivalent.

$(V_{GS} \leftarrow V_T) \rightarrow SLOW OFF$

- When the gate-to-source voltage is less than the threshold value, the MOSFET is OFF.
- When the gate-to-source voltage is greater than the threshold value, the MOSFET is ON.
- When V_{GS} is varied between $V_{GS(th)}$ and $V_{GS(on)}$, the MOSFET is being operated as a switch.

* MOSFET as an Amplifier:-

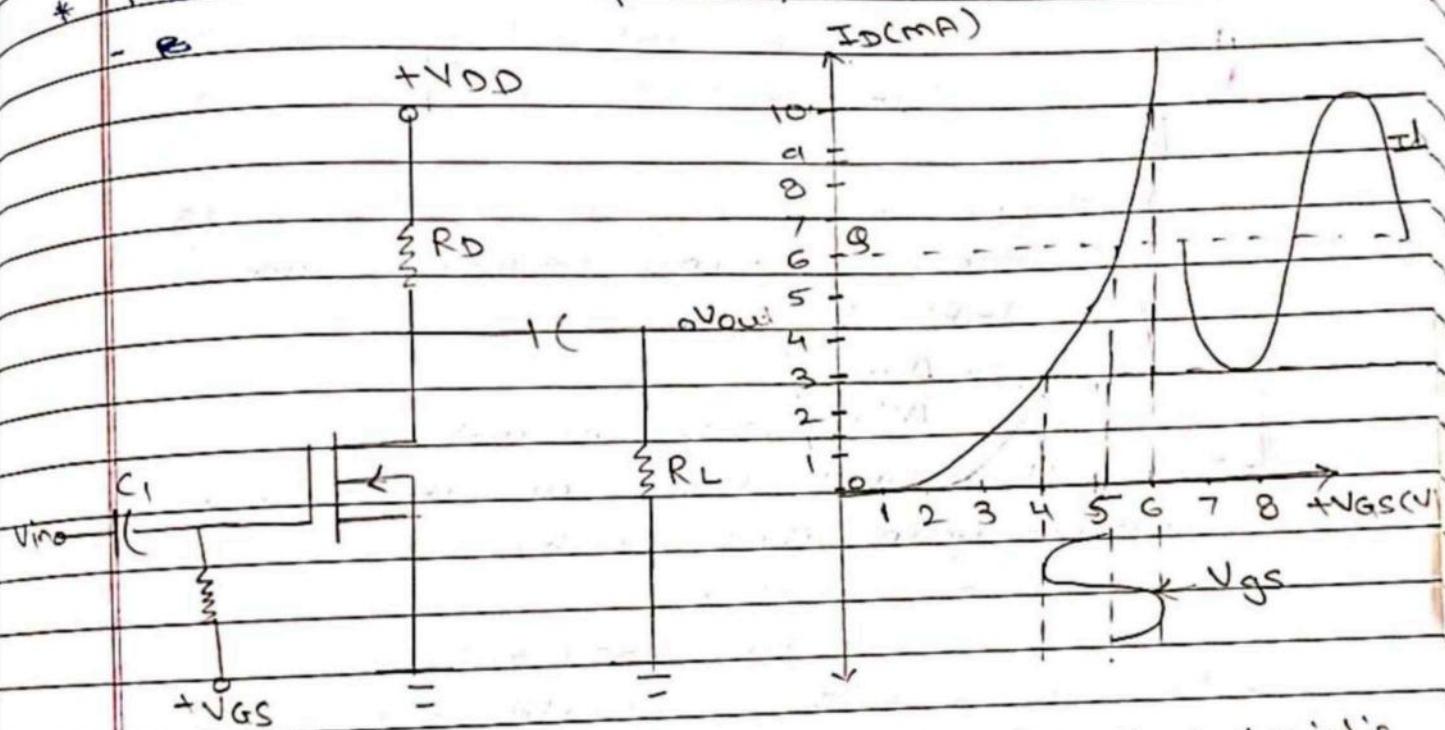

CS MOSFET amplifier Transfer characteristics

- Fig. shows a common source amplifier using n-channel D-MOSFET. Here, the source terminal is common to the input and output terminals and hence the name.
- The amplifier circuit is positive biased (i.e. $V_{GS} = 5V$) with an a.c. source coupled to the gate through the coupling capacitor C_1 .
- When a.c. input signal is absent, the gate is at 5V d.c. and the source terminal is grounded, thus $V_{GS} = 5V$.