

JOIN **PUNE ENGINEERS** **PUNE ENGINEERS** **WHATSAPP CHANNEL**

All Subject Notes:

<https://www.studymedia.in/fe/notes>



JOIN COMMUNITY OF 30K+ ENGINEERS

CLICK HERE TO JOIN



SCAN ME



Ques. No.	Sub Q. No.							Total Marks
Examiner	Marks							
Moderator	Marks							

5

P. No.
Q. No.

B]

AC


FUNDAMENTALS

6

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. क्र.
Q. No.

generation of 1φ AC

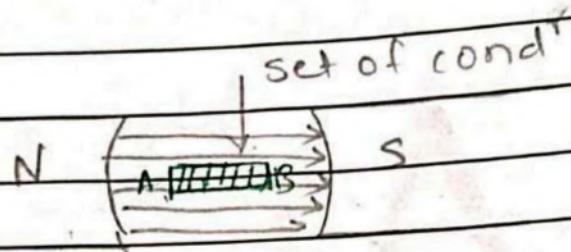

$$e = -N \frac{d\phi}{dt}$$

Anti clockwise - rotation.


velocity - ω rad / sec

Sub Q. No.						Total Marks
niner	Marks					
generator	Marks					

23

Concept of AC & DC Quantities

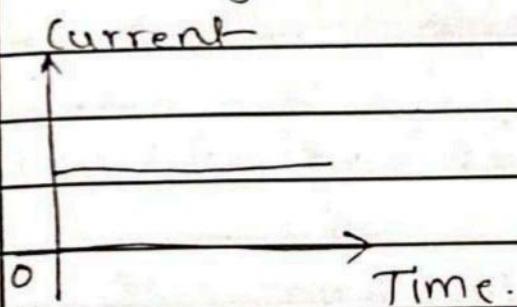
DC - Direct current has constant value (magnitude) with respect to time. Polarity (direction) do not change with time.



AC :

'Alternating current is the current whose magnitude and direction change with the time.'

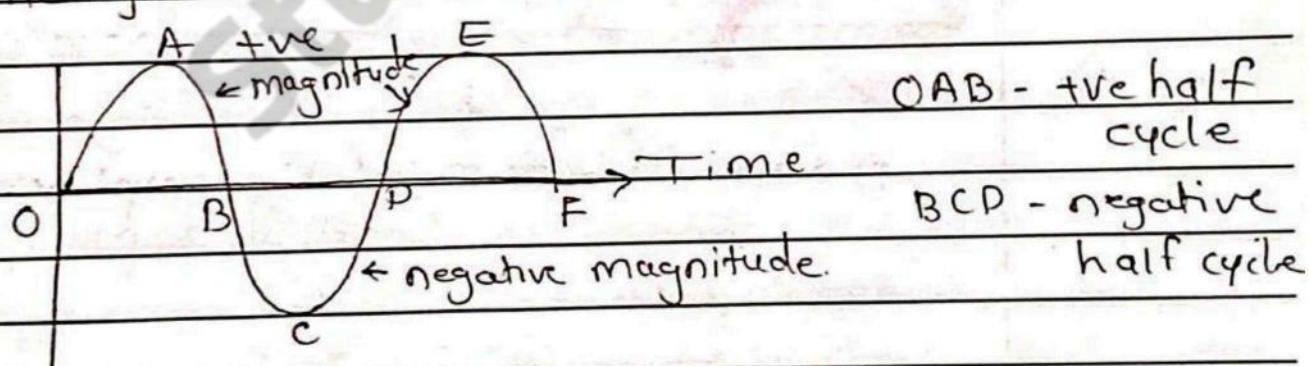Ac keep on alternating +ve & -ve during one cycle.



Advantages:

- Generation is easy and cheaper
- Using x'mer easily ↑ & ↓
- Ac generator have higher η than dc generator
- Negligible loss of energy during transmission
- Ac can be easily converted to DC. (Rectifier)


24.

Muc. No.	Sub Q. No.					
Examiner	Marks					
Moderator	Marks					

प्र. क्र.
Q. No.


→ Graphical Representation of sinusoidal voltage and current

max +ve amplitude

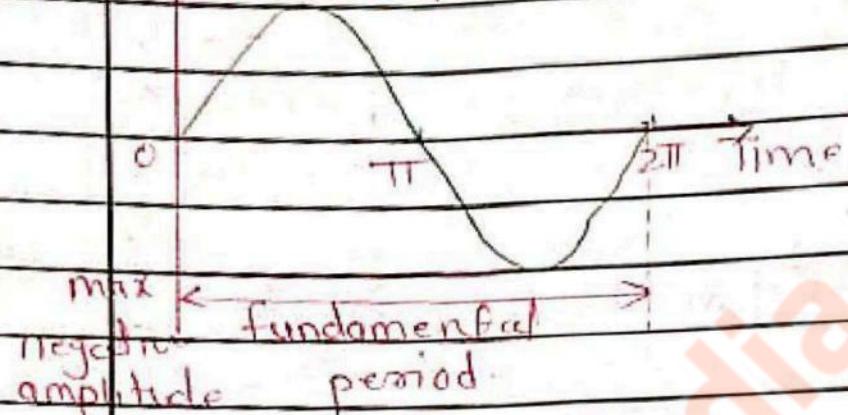


* Diff. types of Waveform.

amplitude

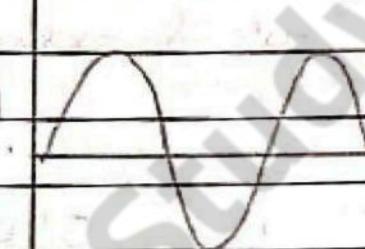


a) sine waveform

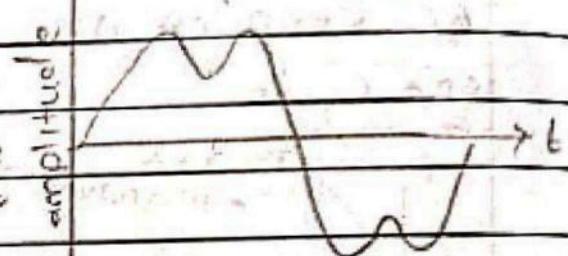


b) complex waveform

c) Triangular waveform

amplitude

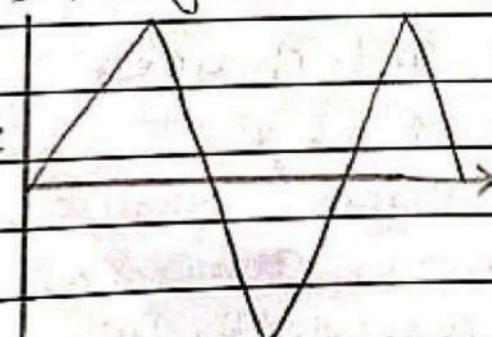

d) square waveform

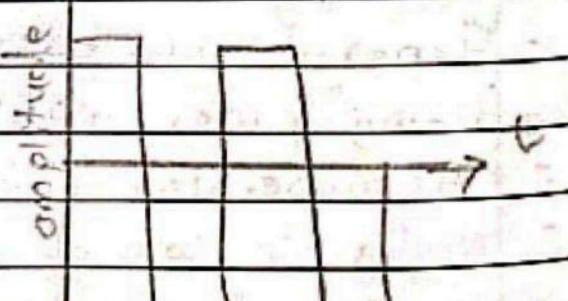

Ques. No.	Sub Q. No.					Marks
Examiner	Marks					
Moderator	Marks					

25


* Single phase Alternator

* Generation of alternating voltage

Angle	Flux cutting	emf or current
-------	--------------	----------------

- i) $\theta = 0^\circ$ No flux cutting zero
- ii) $\theta = 0$ to 90° flux cutting \uparrow from emf \uparrow from 0 to maximum maximum.
- iii) $\theta = 90^\circ$ max. flux cutting max. +ve value
- iv) $\theta = 90$ to 180° flux cutting \downarrow emf start reducing reduced from max to 0. from max to 0.
- v) $\theta = 180^\circ$ No flux cutting zero
- vi) $\theta = 180^\circ$ to 270° flux cutting in reverse direction emf \uparrow in reverse direction
- vii) $\theta = 270^\circ$ max. flux cutting max negative emf in reverse direction
- viii) $\theta = 270^\circ$ to 360° flux cutting reduce to zero emf reduces to zero
- ix) $\theta = 360^\circ$ No flux cutting zero.

max (+ve)

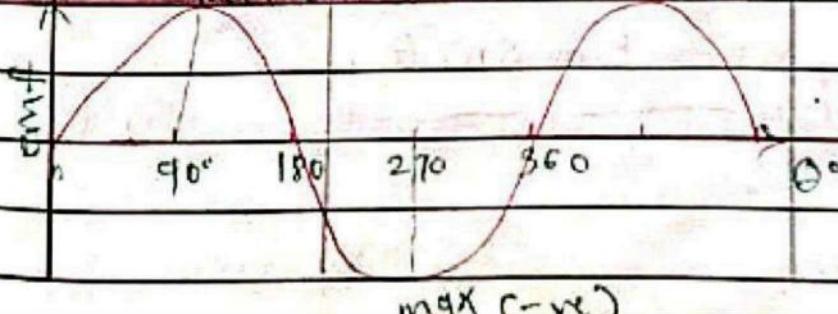

26

Que. No.		Sub Q. No.						Total Marks
Examiner	Marks							
Moderator	Marks							

प्र. क्र.
Q. No.

* Equations of Alternating Voltage and current.

i) While generating a sinusoidal voltage (emf) a cond^r is rotated in mag. field. Here θ is an angle th^r which cond^r is rotated. According to Faraday's law, electromagnet induction, generated emf is given by,

$$e = B \cdot l \cdot v \sin \theta \quad \text{--- (1)}$$

B = flux density of mag. field.

l = length of conductor

v = velocity of rotation of coil.

We discussed, max emf is generated when angle θ is 90° . The max(peak) emf is denoted by E_m

$$E_m = B l v \sin (90^\circ) \quad \text{--- (2)}$$

$$\sin 90^\circ = 1$$

$$E_m = B l v \quad \text{--- (2)}$$

put value of (2) in (1)

we get

$$e = E_m \sin \theta$$

	Sub Q. No.					Total Marks
Miner	Marks					
Erator	Marks					

3

* Different forms of voltage equation.

θ is angle th' which cond' is rotated.
It can be expressed in terms of angular (ω) i.e. frequency (ω), as

$$\theta = \omega t$$

$$e = E_m \sin \theta$$

$$e = E_m \sin \omega t \quad \text{--- (3)}$$

- If the coil angle is ϕ then eqn of voltage is

$$e = E_m \sin (\omega t + \phi)$$

This eqn in terms of max. voltage and coil angle.

$$\text{angular frequency } (\omega) = 2\pi f$$

$$\therefore e = E_m \sin (2\pi ft) \quad \text{--- (4)}$$

This is equation in term of frequency

- The frequency is reciprocal of time period.

$$f = \frac{1}{T}$$

$$\therefore e = E_m \sin \left(\frac{2\pi t}{T} \right)$$

This is equation in term of period.

W/ No.	Marks							Total Marks
Examiner	Marks							
Moderator	Marks							

5

Instantaneous value:

The value (magnitude) of alternating quantity at a particular time instant, is called as instantaneous value.

Cycle

Each repetition of one positive and one negative portion of waveform is called as cycle.

Period (T)

The time taken by alternating quantity to complete one cycle is called period of waveform.

Amplitude:

The max. value attained by alternating quantity is called as amplitude.

$$(-V_m \text{ to } +V_m)$$

Frequency: (f)

The no. of cycles completed by alternating quantity per second, is called as frequency.

$$T = \frac{1}{f} \quad \text{or} \quad f = \frac{1}{T}$$

6

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. क्र.
Q. No.Angular frequency / velocity (ω)

Angular frequency or angular velocity is frequency expressed in electrical radian per second.

$$\omega = 2\pi f \text{ rad/sec}$$

* Peak to peak value

The voltage measured from max. negative level ($-V_m$) to maximum positive voltage level (V_m) is called peak to peak voltage.

(It helpful to decide safe operating region of the device.)

* Effective or RMS value

RMS value of ac current is equal to the d.c current flowing th' given circuit for a given time, producing same amount of heat as produced by ac current flowing th' the same ckt & for the same time

* The square root of mean value of squares of alternating quantity over one cycle.

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						


23

Q. No.
O. No.

* RMS value in terms of peak value
(Derivation)

- Step I) Draw a waveform & write math. eqn
- ii) Cal. square of current I^2 .
- iii) Cal. average value of square equation of Step II.
- iv) Cal. square root of average value. It gives rms value.

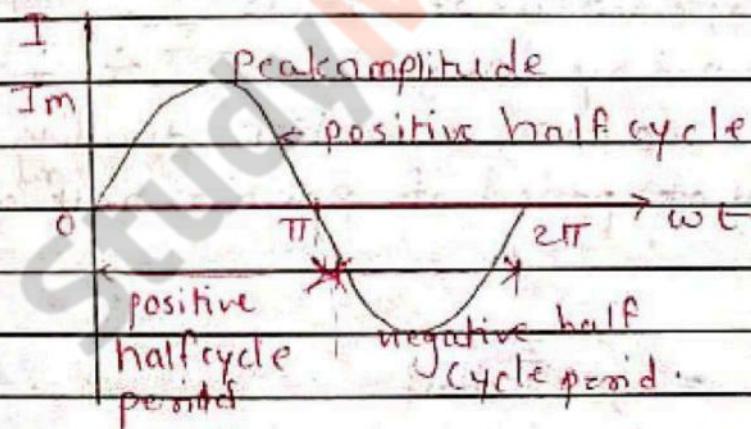- Step I) Draw a wave form & write mathematical equation.



$$I = I_m \sin \omega t \quad \text{Time} \rightarrow \textcircled{1}$$

↑ peak amplitude ↑ angular velocity

- Step II: Cal. the square of current taking square of eqⁿ ①

$$I^2 = I_m^2 \sin^2 \omega t$$

24.

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. नं.
Q. No.

$$\sin^2 \omega t = \frac{1 - \cos 2\omega t}{2} \quad (\text{mathematically})$$

$$I^2 = I_m^2 \left[\frac{1 - \cos 2\omega t}{2} \right]$$

$$\boxed{I^2 = \frac{I_m^2}{2} [1 - \cos 2\omega t]} \quad \text{--- (2)}$$

III) Cal. average value (I_{av}^2)

Average value of I^2 is I_{av}^2 . It is obtained by integrating I^2 for one half cycle (0 to π) and then dividing it by period of one half cycle (0 to π)

$$I_{av}^2 = \int_0^{\pi} I^2 dt$$

$$= \int_0^{\pi} \frac{I_m^2}{2} [1 - \cos(2\omega t)] dt$$

$$= \frac{I_m^2}{2\pi} \int_0^{\pi} 1 - \cos(2\omega t) dt$$

Sub Q.No.					Total Marks
Inner Marks					
Outer Marks					

25

$$= \frac{I_m^2}{2\pi} \left[\int_0^\pi 1 dt - \int_0^\pi \cos 2\omega t dt \right]$$

$$= \frac{I_m^2}{2\pi} \left[(\omega t)_0^\pi - \left[\frac{\sin 2\omega t}{2} \right]_0^\pi \right]$$

$$= \frac{I_m^2}{2\pi} \left[(\pi - 0) - \left[\frac{\sin(2\pi) - \sin 0}{2} \right] \right]$$

$$= \frac{I_m^2}{2\pi} \left[(\pi - 0) - \left[\frac{\sin(2\pi) - \sin(0)}{2} \right] \right]$$

$$I_{av} = \frac{I_m^2}{2}$$

Tr) Step 4) Cal. RMS value

RMS value of current is denoted by I_{rms} . It is obtained by taking square root of I^2 .

$$\therefore I_{rms} = \sqrt{\frac{I_m^2}{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$I_{rms} = 0.707 I_m$$


26

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

R. No.
Q. No.

Derivation of Average value in term
of peak value

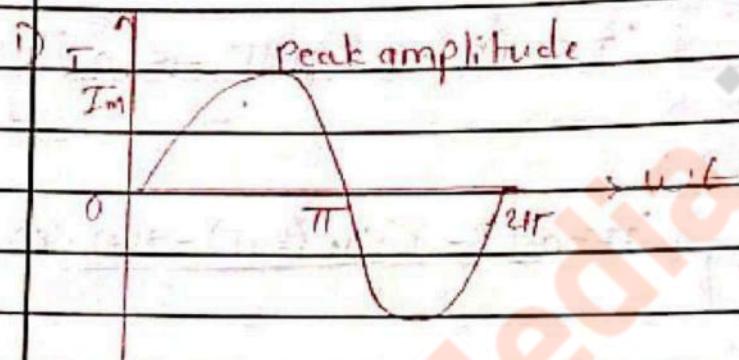- i) Draw waveform & write math. eqn.
ii) Cal. average value



$$I = I_m \sin wt$$

ii) Cal. average value

It is obtained by integrating the half cycle & then dividing it by the full cycle.

$$I_{av} = \frac{1}{T} \int_0^T I \cdot dt$$

$$= \frac{1}{T} \int_0^{\pi} I_m \sin wt \cdot dt$$

$$I_{av} = \frac{I_m}{\pi} \int_0^\pi \sin \omega t \, d\omega t$$
$$= \frac{I_m}{\pi} \left[-\cos \omega t \right]_0^\pi$$

$$I_{av} = \frac{I_m}{\pi} \left[-\cos(\pi) - (-\cos(0)) \right]$$

$$I_{av} = \frac{I_m}{\pi} [1+1]$$

$$I_{av} = \frac{2 I_m}{\pi}$$

$$I_{av} = 0.637 I_m$$

* Form Factor.

The ratio of rms value to average value of an alternating quantity is called form factor.

$$K_f = \frac{\text{rms value}}{\text{average value}}$$

For sin / cosine quantity

$$K_f = 0.707 I_m$$

$$0.637 I_m$$

$$K_f = 1.11$$

4

Que. No.	Sub Q. No.					Total Marks
Examiner	Marks					
Moderator	Marks					

प्र. क्र.
Q. No.

* Peak factor or Crest factor (k_p)

The ratio of max (peak) value to the rms value of an alternating quantity is called crest factor.


$$k_p = \frac{\text{Peak value}}{\text{rms value}}$$

Basic eq'

$$k_p = \frac{I_m}{0.707 I_m} = 1.414$$

for sinusoidal quantity.

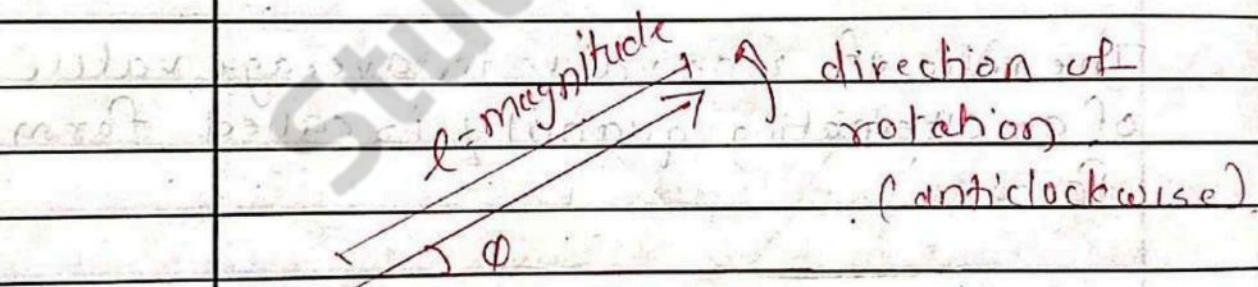* Phasor representation of sinusoidal quantities




Phasor representation is a simple method to represent alternating quantities such as sine wave, cosine wave.

$$I_m = \sqrt{2} I_{\text{rms}}$$


	Sub Q. No.					Total Marks
Generator	Marks					
Generator	Marks					

5

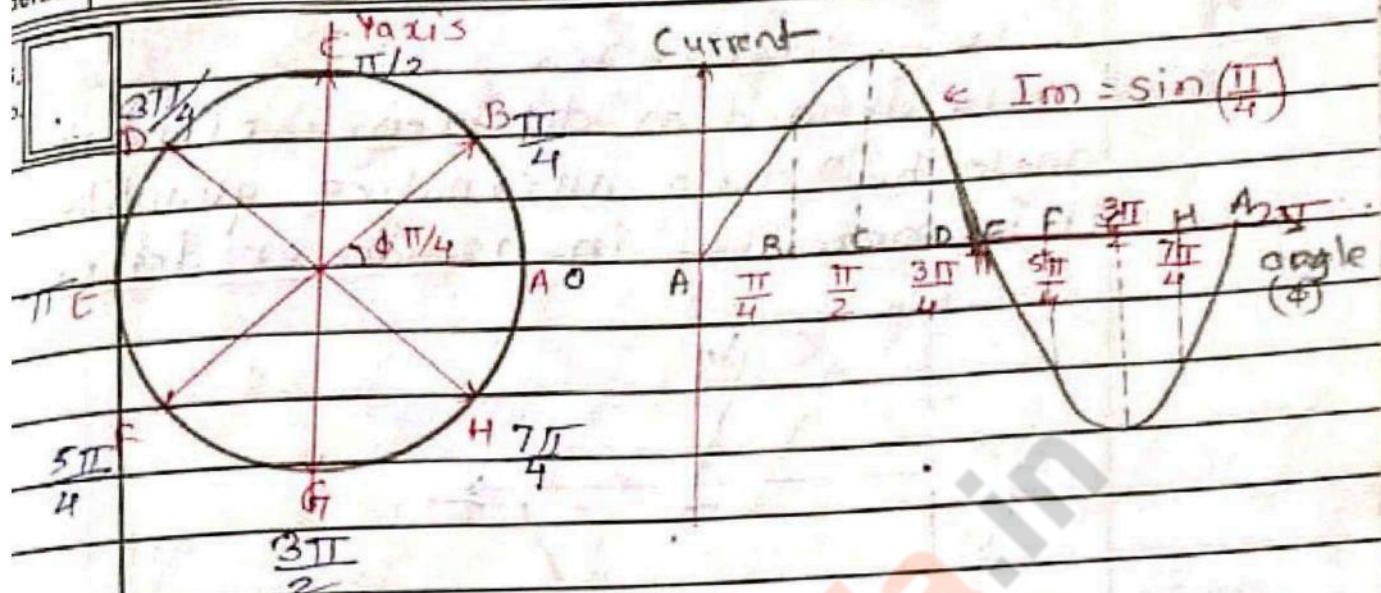


* Phase / phase angle

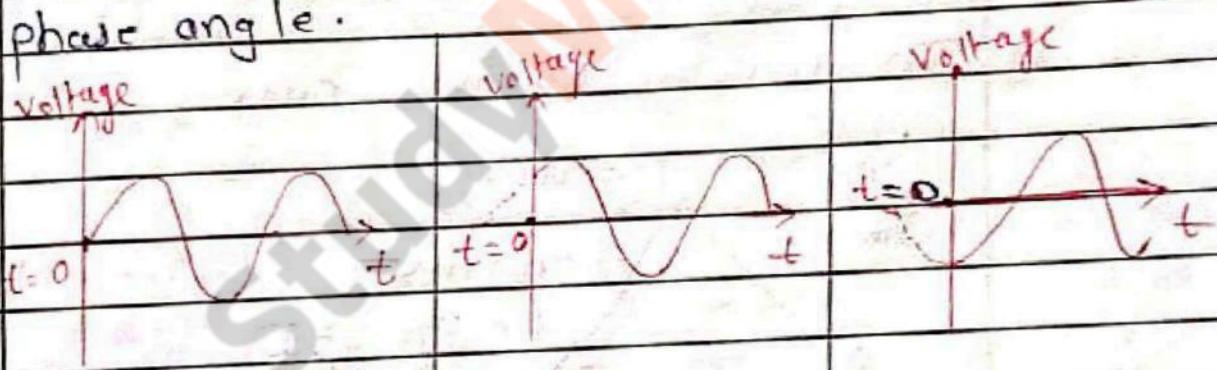A position of phasor at a particular instant is expressed in term phase or phase angle.



$$V = V_m \sin \omega t$$

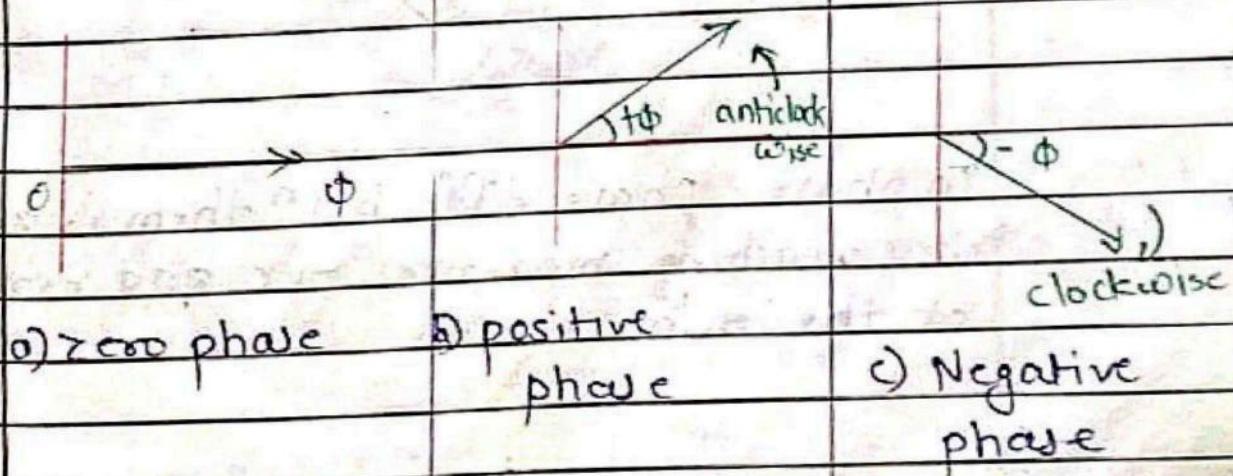


6

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. क्र.
Q. No.


phase difference

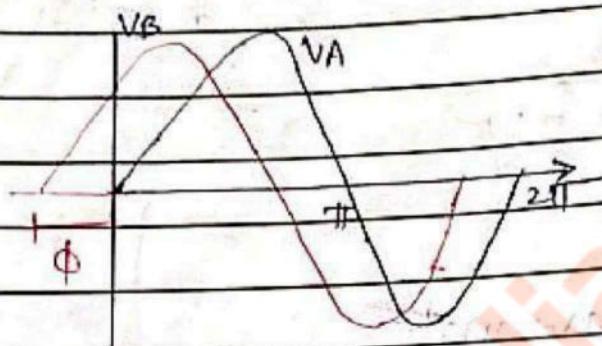It is defined as difference of phase angle bet'n two alternating quantities
It is measured in radian or degree.



* Type of phase difference

i) In phase or zero phase

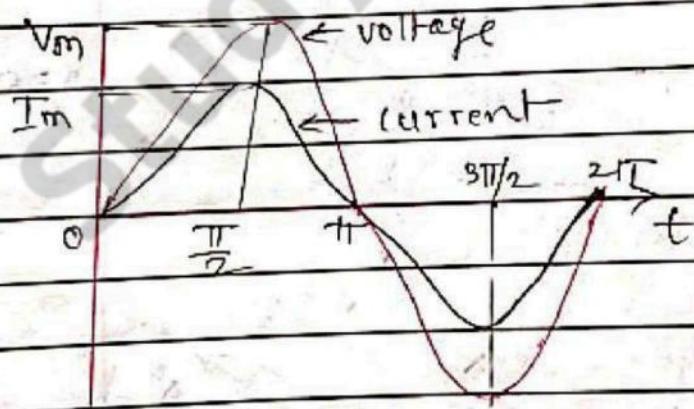


In phase - phase diff. bet'n them is zero
They reaching max +ve, -ve and zero value at the same time.

	Sub Q. No.					Total Marks
Miner	Marks					
Arator	Marks					


23

2) Out of phase

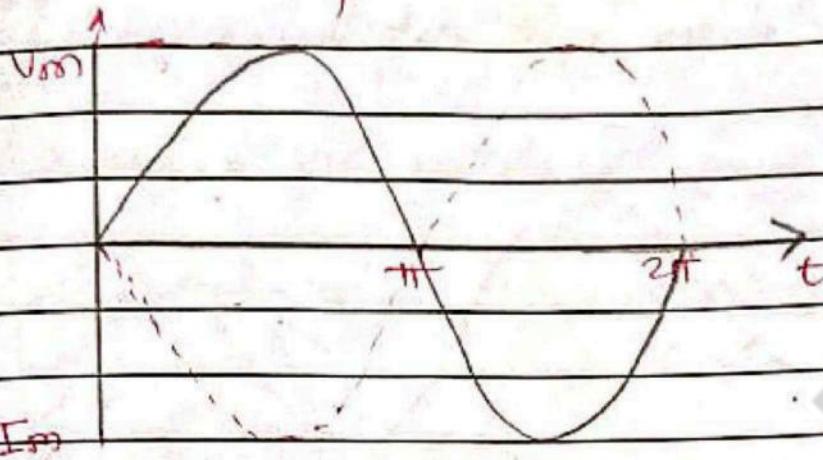

- They are said to out of phase when phase diff. is 180°

3) Leading phase

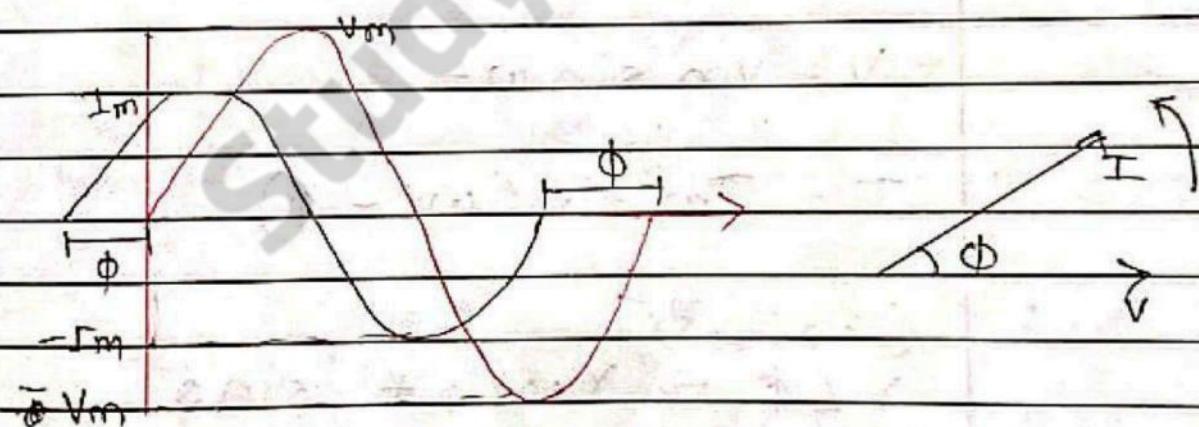

- Current waveform reaches its max. min } zero value prior to voltage waveform
So these two having leading phase diff.

$$V = V_m \sin \omega t$$

$$I = I_m \sin(\omega t + \phi)$$


I lead to V by angle ϕ

24.

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. नं.
Q. No.

4) Lagging phase

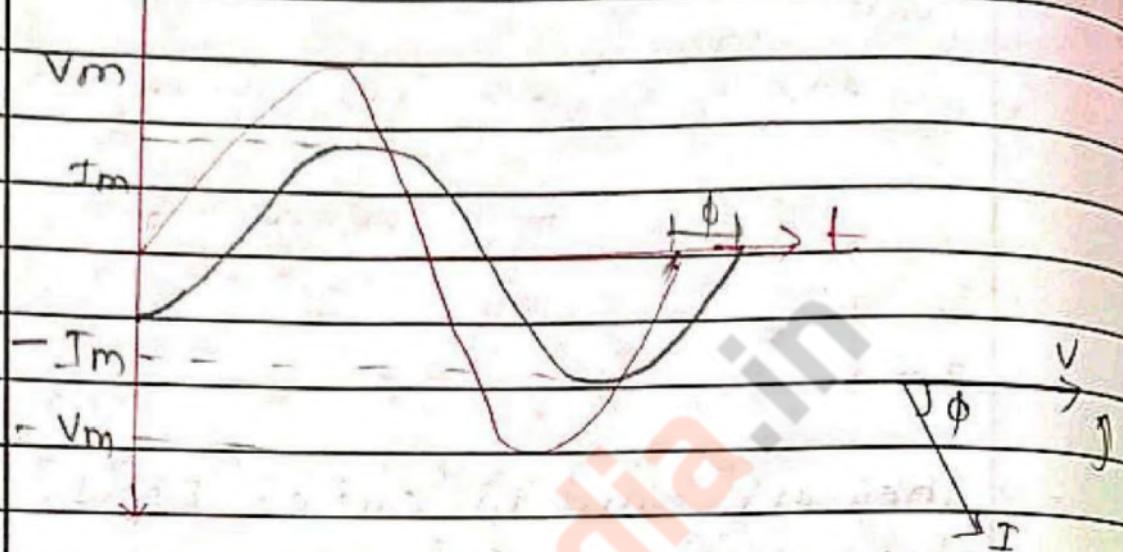

- Here current waveform reaches its max +ve, -ve & zero value later than voltage waveform.

$$V = V_m \sin \omega t$$

$$I = T_m \sin(\omega t - \phi)$$

Conversion

$$r / \phi \rightarrow r \cos \phi + j \sin \phi$$

Polar \rightarrow rectangular


$$x + jy \Rightarrow r L \phi = \sqrt{x^2 + y^2} \angle \tan^{-1} \frac{y}{x}$$

Sub Q. No.						Total Marks
Marks						
Marks						

25

* Rectangular & Polar representation of phasor - Basically phasor contain magnitude & angle. Two methods to represent phasor:

1) Polar Representation.

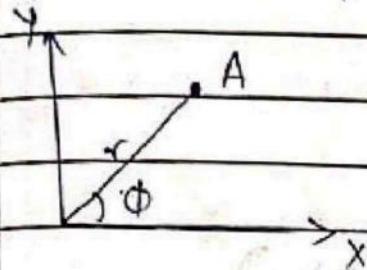


$$V = V_m \sin(\omega t + \phi)$$

$$V_m = r$$

$$V = r / \phi$$

2) Rectangular Representation.

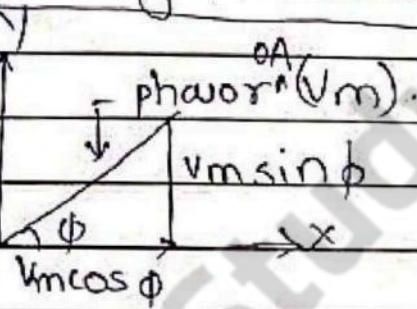

$$V(t) = x + jy$$

Here

$$x = V_m \cos \phi, y = V_m \sin \phi$$

$$V_t = V_m \cos \phi + j V_m \sin \phi$$

e.g. $i = 5 \sin(100\pi t + 30^\circ)$

$\text{Im}(i)$ $\omega = \phi$

polar representation $= r / \phi = 5 / 30^\circ$

Rectangular representation

$$= r \cos \phi + j r \sin \phi$$

$$= 5 \cos 30^\circ + j 5 \sin 30^\circ$$

$$= 4.33 + j 2.5$$

26

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. क्र.
Q. No.

* Addition & Subtraction of phasor.

- always in rectangular form.

$$A = x_1 + jy_1$$

$$B = x_2 + jy_2$$

$$A+B = (x_1+x_2) + j(y_1+y_2)$$

$$A-B = (x_1-x_2) + j(y_1-y_2)$$

* Multiplication & Division of phasor.

- always in polar form.

$$A_1 = r_1 \angle \phi_1$$

$$B = r_2 \angle \phi_2$$

$$A \bar{X} B = r_1 \times r_2 / (\phi_1 + \phi_2)$$

$$A = r_1 \angle (\phi_1 - \phi_2)$$

$$B = r_2$$

Sub Q.No.							Total Marks
er	Marks						
or	Marks						

3

Cal.

mode - 2 complex

polar to Rect

Rect to polar

fx 991 ES

Sub Q. No.						Total Marks
Examiner	Marks					
Moderator	Marks					

25

AC Fundamental (Numerical)

- 1) A 50 Hz sinusoidal voltage has rms value of 200V. At $t = 0$, the instantaneous value is +ve and half of its max. value. Write down the expression for voltage and sketch the waveform.

→ Given,

$$F = 50 \text{ Hz}$$

$$V_{\text{rms}} = 200 \text{ V}$$

$$V_m = \sqrt{2} V_{\text{rms}} = \sqrt{2} \times 200 = 282.84 \text{ V}$$

Expression for instantaneous voltage

$$V(t) = V_m \sin(\omega t + \phi) \quad \text{--- (1)}$$

To cal. ϕ , we will consider voltage at $t = 0$.

At $t = 0$

$$V(0) = \frac{V_m}{2} = \frac{282.84}{2} = 141.42 \text{ V}$$

put this value in eq (1) at $t = 0$.

$$141.42 = 282.84 \sin(0 + \phi)$$

$$\sin \phi = \frac{141.42}{282.84} = 0.50$$

$$\phi = \sin^{-1}(0.5) = \frac{\pi}{6} (30^\circ) (\text{from table})$$

26

Que. No.	Sub Q. No.							marks
Examiner	Marks							
Moderator	Marks							

प्र. क्र.
Q. No.

$$\omega = 2\pi f = 2\pi \times 50 = 100\pi$$


put values of V_m , ω & ϕ in eqⁿ (1)

$$V(t) = 282.84 \sin(100\pi t + \frac{\pi}{6})$$

$$V_C(t) = 282.84 \sin(100\pi t + \frac{60^\circ}{30^\circ})$$

This is expression of voltage

ii) sketch the waveform

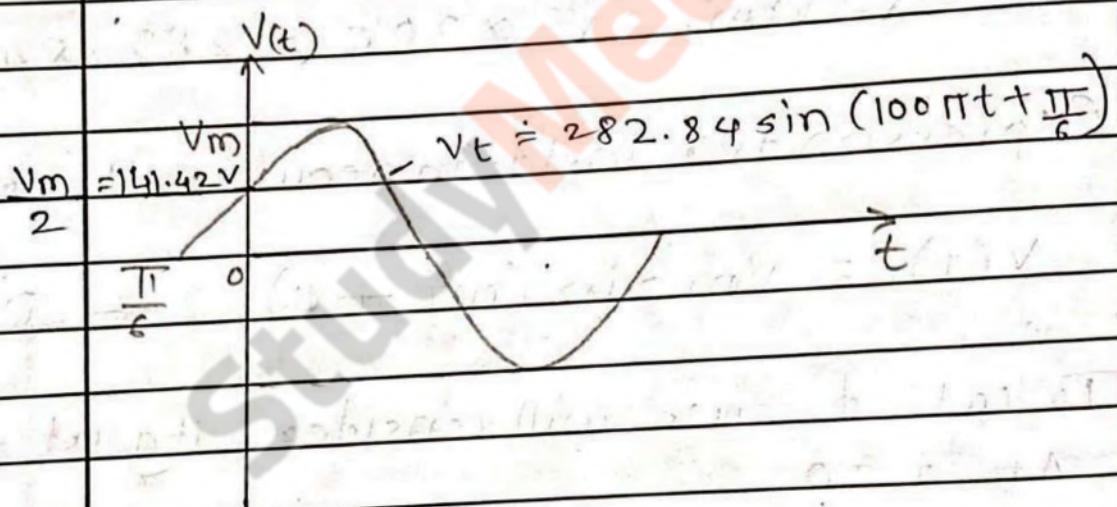

The waveform is sinusoidal

At $t = 0$, amplitude is $V_m = 141.42 \text{ V}$

The phase shift is positive $\frac{\pi}{6}$ rad (30°)

Ques. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

3

2. The RMS value of 50 Hz sinusoidally varying current is 20A. When $t=0$, its value is 10A. Obtain equation of current. Find the value of current when $t=0.0025\text{ sec}$. Also sketch the wave form.

→ Given :

$$f = 50\text{ Hz}$$

$$I_{\text{rms}} = 20\text{ A} \quad 30\text{ A}$$

$$\text{At } t=0, I_{\text{rms}} = 10\text{ A} \quad 15\text{ A}$$

i) Equation of current

$$i(t) = I_m \sin(\omega t + \phi)$$

Here,

$$I_m = \sqrt{2} I_{\text{rms}} = \sqrt{2} \times 20 = 28.28 \text{ A}$$

$$\text{and } \omega = 2\pi f = 2\pi \times 50 = 100\pi$$

$$i(t) = 28.28 \sin(100\pi t + \phi) \quad \text{--- (1)}$$

ii) Calculate ϕ .

$$\text{At } t=0, I_{\text{rms}} = 10\text{ A}, i(t) = \sqrt{2} \times I_{\text{rms}} \\ = \sqrt{2} \times 10 = 14.14 \text{ A}$$

$$t=0.$$

$$10 = 28.28 \sin(0 + \phi)$$

$$\sin \phi = \frac{10}{28.28} = 0.35$$

4

Que. No.	Sub. Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. क्र.
Q. No.

$$\phi = \sin^{-1} 0.5 = \frac{\pi}{6} \text{ (in radian mode)}$$

$$\phi = 30^\circ$$

3) Cal. i at $t = 0.02 \text{ sec.}$

$$i(t) = \underline{28.28 \sin(100\pi t + 30^\circ)}$$

$$i(t) = 28.28 \sin(100\pi \times 0.02 + 30^\circ)$$

$$i_t = 28.28 \sin(2\pi + 30^\circ)$$


$$i(t) = 28.28 \left[(\sin 2\pi) + (\sin 30^\circ) \right]$$

$$i(t) = 28.28 (0.5)$$

$$i(t) = 14.14 A$$

equation of current

$$i = 28.28 \sin(100\pi t + 30^\circ)$$

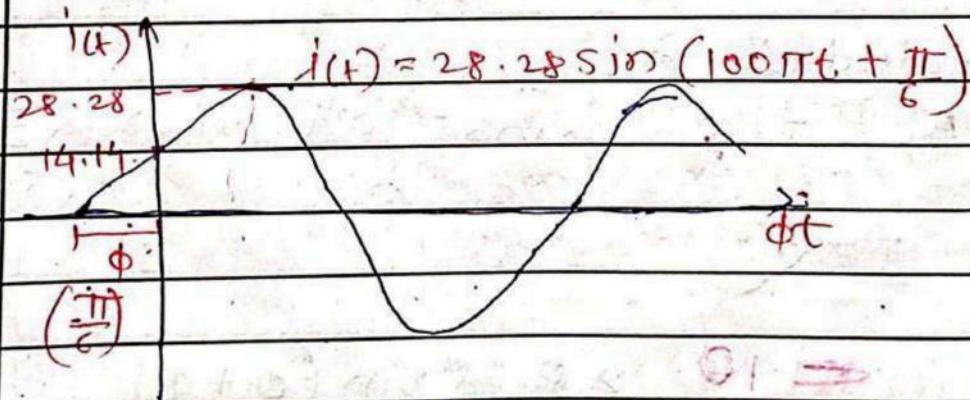

Due No.	Sub Q. No.					Total Marks
Examiner	Marks					
Moderator	Marks					

5

3.

A sinusoidally varying a.c voltage is given by $v = 141.4 \sin(100\pi t)$ volts. Find (i) Rms, (ii) average value, (iii) freq.

→ Given

$$v = V_m \sin \omega t$$

$$v = \frac{141.4}{V_m} \sin 100\pi t$$

i) Rms value. V_{rms} .

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 99.98 \text{ V}$$

ii) Cal. of avg. value.

$$V_{av} = 0.637 V_m$$

$$= 0.637 \times 141.4$$

$$V_{av} = 90.0718 \text{ V}$$

iii) freq.

$$\omega = 2\pi f$$

$$100\pi = 2\pi f$$

$$f = \frac{100\pi}{2\pi}$$

$$f = 50 \text{ Hz}$$

5

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

क्र. No.

1)

An alternating current varying sinusoidally with a freq. 50 Hz has a rms value of 10 A. Write down eqn inst value of this current quantity and find its value for $t = 0.0015 \text{ sec}$ & $t = 0.0075 \text{ sec}$ after passing thr zero the increasing negatively.

→

Given

$$f = 50 \text{ Hz}, I_{\text{rms}} = 10 \text{ A}$$

$$t_1 = 0.0015 \text{ msec}$$

$$t_2 = 0.0075 \text{ msec}$$

$$i = I_m \sin \omega t$$

$$I_m = \sqrt{2} I_{\text{rms}} = \sqrt{2} \times 10 = 14.14 \text{ A}$$

equation for instantaneous value of i

$$i(t) = I_m \sin \omega t$$

$$= 14.14 \sin(2\pi f) \cdot t$$

$$i(t) = 14.14 \sin(2\pi \times 50)t$$

$$i(t) = 14.14 \sin(100\pi)t \quad \text{--- (1)}$$

1) $i(t) = ? \text{ when } t = 0.0015 \text{ msec}$

$$i(t) = 14.14 \sin(100\pi) \times 0.0015$$

$$= 14.14 \times (-0.86) = -12.14$$

$$= -12.14 \text{ A}$$

Sub Q. No.						Total Marks
er	Marks					
or	Marks					

23

when $t = 0.0075$

$$I(t) = Im \sin wt \\ = 14.14 \sin (100\pi \times 0.0075)$$

$$I(1) = -0.7888 \text{ A} = -10 \text{ A}$$

24.

Que. No.	Sub Q. No.						Total Marks
Examiner	Marks						
Moderator	Marks						

प्र. क्र.
Q. No.

2.

A sinusoidally varying alternating voltage of 100V (RMS value) with 50Hz freq. is applied to a clc. find.

- a) mathematically eqn of voltage
- b) time period
- c) The inst. value of voltage at $t = 1.667 \text{ ms}$
- d) The time when inst. voltage is 100V
- e) V_{avg} . f) V_m .

→ Given.

$$V_{\text{rms}} = 100 \text{ V}$$

$$f = 50 \text{ Hz}, \omega = 2\pi f, \omega = 100\pi$$

- a) equation of voltage.

$$V_m = V_{\text{rms}} \times \sqrt{2}$$

$$= 100 \times \sqrt{2}$$

$$V_m = 141.42 \text{ V}$$

$$V(t) = V_m \sin \omega t$$

$$= 141.42 \sin \omega t (100\pi)t$$

b) time period (T) $= \frac{1}{f} = \frac{1}{50} = 0.02 \text{ sec.}$

c) $V(t)$ when $t = 1.667 \text{ ms}$

$$V(t) = 141.42 \sin (\omega) \times 1.667 \times 10^{-3}$$

$$V(t) = 141.42 \sin (100\pi) \times 1.667 \times 10^{-3}$$

Sub Q. No.						Total Marks
Inner Marks						
Outer Marks						

25

$$V(t) = 70.72 V$$

d) $t = ?$ when $V(t) = 100 V$.

$$V(t) = 141.42 \sin(100\pi)t$$

$$100 = 141.42 \sin(100\pi)t$$

$$\sin(100\pi t) = \frac{100}{141.42}$$

$$\sin 100\pi t = 0.707$$

$$t = \frac{\sin^{-1} 0.707}{100\pi}$$

$$t = \frac{0.785}{100\pi} \text{ sec}$$

$$2.5 \times 10^{-3} \text{ sec}$$

e) $V_{avg} = ?$

$$V_{avg} = 0.637 V_m$$

$$V_{avg} = 0.637 \times 141.42$$

$$V_{avg} = 90.08 V$$

f) $V_m = 141.42 V$

III

Single phase AC Circuits.

M	T	W	F	S	S
Page No.:	1				
Date:					FIDNA

- R, L, C circuit Elements:

AC Circuit

- AC Fundamentals
- Pure R
 - Pure L
 - Pure C.

- AC Series circuit
- $R + L$
 - $R + C$
 - $R + L + C$

1. Basic three elements are used in AC circuits.
 - 1) Resistor (R)
 - 2) Inductor (L)
 - 3) Capacitor (C)
- We will discuss AC response of following circuit.
 1. Purely resistive AC circuit
 2. Purely inductive AC circuit
 3. purely capacitive AC circuit.

In this cases, we will assume the equation of the applied voltage


$V = V_m \sin \omega t$ & determine current equation in the following steps:

1. Draw a circuit diagram
2. Establish equation of current 'i'
3. Draw waveform of v & i
4. Draw phasor diagram of v & i
5. Determine 'opposition' to the current flow.
6. Determine phase angle (p.f.angle) between v & i

7. Determine power factor of circuit
8. Determine power consumed by the circuit

* Purely Resistive AC Circuit

I) Circuit diagram:

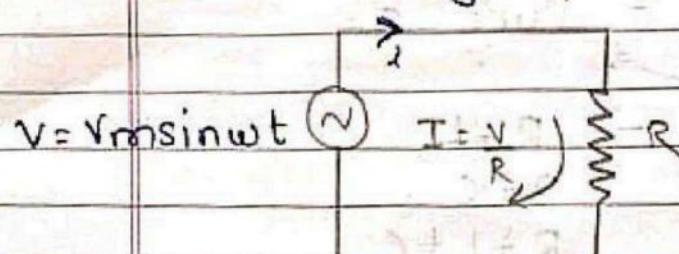

2) Current Equation

applied voltage, $V = V_m \sin \omega t$ — ①

The basic equation of current.

ohm's law, $V = IR$

$$I = \frac{V}{R} = \frac{V_m \sin \omega t}{R}$$

$$\therefore I = \left(\frac{V_m}{R}\right) \sin \omega t \quad \text{--- ②}$$

eqn ② is instantaneous equation of current for purely resistive AC circuit. The std. eqn of current is

$$I = I_m \sin (\omega t + \phi) \quad \text{--- ③}$$

skip
where,

I_m = peak (max) value of current


ϕ = phase difference

Comparing eqn ② & ③, we get


$$I_m = \frac{V_m}{R} \quad \& \quad \phi = 0$$

$$I = I_m \sin \omega t$$

3) Voltage \Rightarrow current waveform.

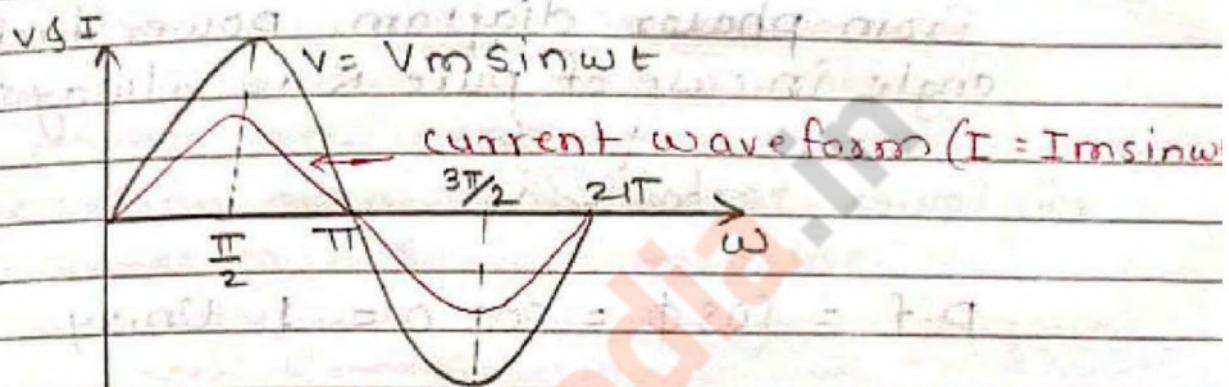

4) phasor Diagram.

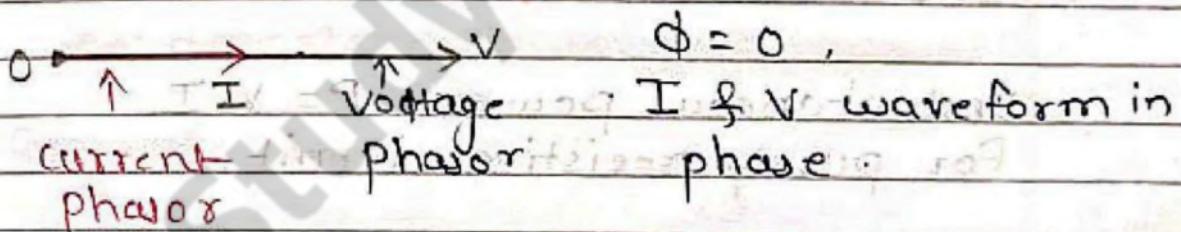

5. Impedance :

1. Rectangular Form : $Z = R + jX$

R = Resistance

jX = Reactance

2. Polar Form : $Z = |Z| \angle \phi$

where, $|Z|$ = magnitude of Z

ϕ = phase difference.

vii) opposition to current flow

$$I_m = \frac{V_m}{R}$$

viii) power factor angle (ϕ) = 0

From phasor diagram, power factor angle in case of pure R is always zero

ix) Power factor:

$$P.f = \cos \phi = \cos 0 = 1 \text{ Unity}$$

ix) Power.

i. Instantaneous Power (P)

ii. Instantaneous power, $P = V \cdot I$

for purely resistive circuit,

$$V = V_m \sin \omega t \quad \& \quad I = I_m \sin \omega t$$

$$\therefore P = V_m \sin \omega t \cdot I_m \sin \omega t$$

$$P = V_m I_m \sin^2 \omega t$$

$$\therefore \sin^2 \omega t = \frac{1 - \cos 2\omega t}{2}$$

$$P = V_m I_m \left[\frac{1 - \cos 2\omega t}{2} \right]$$

$$\therefore P = \frac{V_m I_m}{2} [1 - \cos 2\omega t]$$

$$\therefore P = \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos(2\omega t)$$

constant term fluctuating term

- i) the first term does not contain any sine or cosine component. so it is constant term.
 - ii) The second term contains $\cos(2\omega t)$ so it will change with respect to time. so it is called fluctuating term.

ii) Average Power

- The avg. power of sine wave / cosine wave for one complete cycle is zero.


$$P_{av} = \frac{V_m \cdot I_m}{2}$$

$$2 = \sqrt{2} \times \sqrt{2}. \quad (\text{we can write})$$

$$P_{av} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$


Pav. = Pav. Vrms = Trms. Curwatts = planis

Waveform for Power

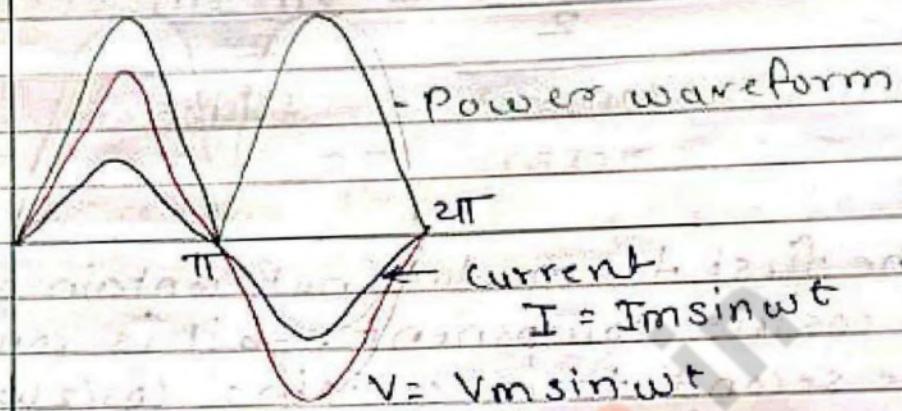

* Purely Inductive Circuit :

- Circuit diagram.

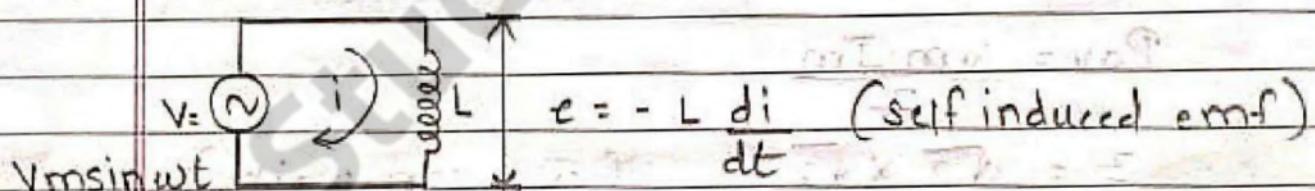

- Current equation.

Supply voltage (V) is equal and opposite to Self induced emf.

$$V = -e = -L \frac{di}{dt} = L \frac{di}{dt}$$

$$\therefore V = V_m \sin \omega t$$

$$\therefore V_m \sin \omega t = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V_m \sin \omega t}{L}$$

equation of current can be obtained by integrating di

$$i = \int di = \int \frac{V_m}{L} \sin \omega t dt$$

$$I = \frac{V_m}{L} \int \sin \omega t dt$$

$$= \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right] = -\frac{V_m}{\omega L} (\cos \omega t)$$

$$\text{Use this, } \cos \omega t = \sin \left(\frac{\pi}{2} - \omega t \right)$$

$$i = -\frac{V_m}{\omega L} \left[\sin \left(\frac{\pi}{2} - \omega t \right) \right]$$

But,

$$\sin \left(\frac{\pi}{2} - \omega t \right) = \sin -\left(\omega t - \frac{\pi}{2} \right) = -\sin \left(\omega t - \frac{\pi}{2} \right)$$

Using identity $\sin(-\theta) = -\sin \theta$.

$$= -\sin \left(\omega t - \frac{\pi}{2} \right)$$

$$i = -\frac{V_m}{\omega L} \left[-\sin \left(\omega t - \frac{\pi}{2} \right) \right]$$

$$i = \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

The term $\frac{V_m}{\omega L}$ is called as peak value I_m

$$I_m = \frac{V_m}{\omega L}$$

$\omega L = X_L = 2\pi f L$ is called reactance of inductance.

$$i = I_m \sin(\omega t - \frac{\pi}{2})$$


ωt = lagging phase, $\frac{\pi}{2}$ = phase shift

- The term $-\frac{\pi}{2}$ indicates that, current in purely inductive circuit lags by $-\frac{\pi}{2}$ or -90° .

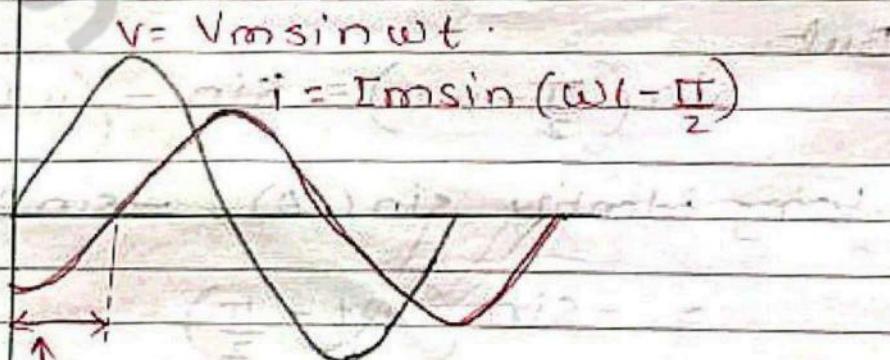(iii) Voltage & Current Waveform.


$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \frac{\pi}{2})$$



phase shift $\phi = \frac{\pi}{2} = 90^\circ$ (lagging).

iv) phasor diagram.

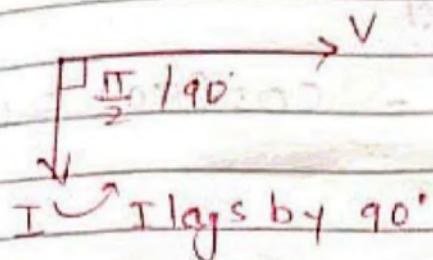

I & V are rms value

v) Impedance:

1) Rectangular form: $Z = R + jX_L$

2) Polar form $Z = \frac{R^2 + X_L^2}{R} \angle \frac{\pi}{2}$


v) Opposition to current flow:

$$X_L = \omega L = 2\pi f L = \frac{2\pi L}{T} \quad \text{if } X_L \text{ is inductive}$$

reactance. Unit - Ω .

for DC $f=0$,

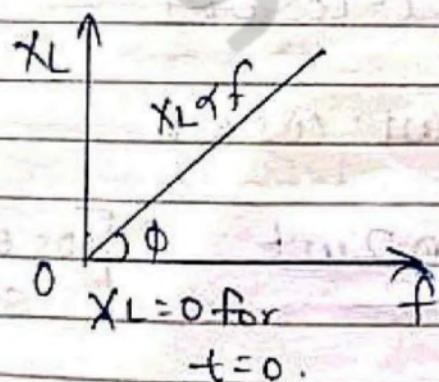$X_L = 0$, hence pure L acts as short ckt.



vii) Power factor angle (ϕ)
 -90° as I lags V .

viii) Power factor = $\cos(90^\circ) = 0$ lagging

ix) Power

Instantaneous Power

$$P = V \times i$$

$$V = V_m \sin \omega t, \quad i = I_m \sin(\omega t - \frac{\pi}{2})$$

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t - \frac{\pi}{2})$$

$$\sin(\omega t - \frac{\pi}{2}) \therefore \sin(\theta - \frac{\pi}{2}) = -\cos \theta$$

$$P = V_m \sin \omega t \cdot I_m \cdot (-\cos \omega t)$$

$$P = V_m I_m \sin \omega t (-\cos \omega t)$$

$$P = -V_m I_m \sin \omega t \cdot \cos \omega t$$

$$\sin \omega t \cdot \cos \omega t = \frac{\sin 2\omega t}{2}$$

$$\left[\cos \theta \cdot \sin \theta = \frac{\sin 2\theta}{2} \right]$$

$$P = -V_m I_m \frac{\sin 2\omega t}{2}$$

$$P = -\frac{V_m I_m}{2} \sin(2\omega t)$$

average power.

$$P_{av} = \frac{2\pi}{0} \int P$$

$$P_{av} = 0.$$

* Purely Capacitive Circuit

1) circuit diagram:



2) Current equation

- Voltage applied to purely capacitive circuit is,
 $V = V_m \sin \omega t$.

The charge q on the plates of capacitor is related to value of capacitor (C)

$$q = Cv = C V_m \sin \omega t$$

- Current is defined as the rate of change of charge,

$$i = \frac{dq}{dt} = \frac{d}{dt} [C V_m \sin \omega t]$$

$$i = C V_m \frac{d}{dt} \sin \omega t$$

$$i = C V_m \omega \cos \omega t$$

$$i = \frac{V_m}{\omega C} \cos \omega t$$

$$\cos \omega t = \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$i = \frac{V_m}{\omega C} \sin \left(\omega t + \frac{\pi}{2} \right)$$

the term $\frac{V_m}{\omega C}$ is denoted by I_m .

$$\frac{1}{\omega C}$$

Here,

$$\frac{1}{\omega C} = X_C \dots \text{reactance of capacitor}$$

$$i = I_m \sin \left(\omega t + \frac{\pi}{2} \right)$$

I_m = peak current


ωt = leading phase

$\frac{\pi}{2}$ = phase shift.


The term $+\frac{\pi}{2}$ indicates that current leads

voltage by $\frac{\pi}{2}$ or 90° .

3) Voltage & Current waveform.

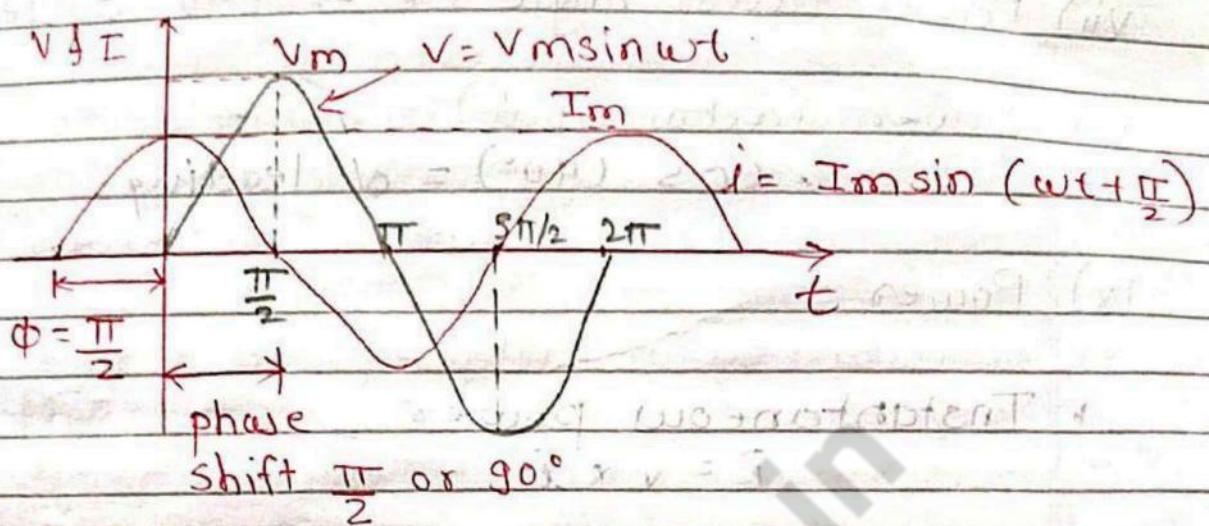

4) phasor diagram

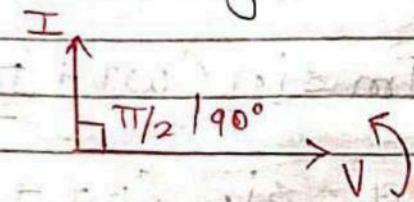

v) Impedance

$$\text{1) Rectangular } z = R + jX$$

$$\text{Polar } z = X_C \angle -\frac{\pi}{2}$$

vi) opposition to current flow

$$\frac{1}{j\omega C} = \frac{1}{2\pi f C}, \quad X_C \text{ called capacitive reactance}$$

$\therefore X_C = \infty$, pure C acts as open circuit.

$$X_C = \frac{1}{j\omega C} = \frac{1}{2\pi f C}$$

$$X_C \propto \frac{1}{f}$$

vii) Power factor Angle (ϕ) $\rightarrow +90^\circ$ as leads V

viii) power factor (p.f.)
 $\cdot \cos(90^\circ) = 0$ leading.

ix) Power

• Instantaneous power

$$P = V \times i$$

$$V = V_m \sin \omega t, i = I_m \sin(\omega t + \frac{\pi}{2})$$

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t + \frac{\pi}{2})$$

$$\therefore P = V_m I_m \sin \omega t \cdot \sin(\omega t + \frac{\pi}{2})$$

$$\left[\sin(\theta + \frac{\pi}{2}) = \cos \theta \right]$$

$$P = V_m I_m \sin \omega t \cdot \cos \omega t$$

$$\sin \theta \cdot \cos \theta = \frac{\sin 2\theta}{2}$$

$$P = V_m I_m \frac{\sin 2\omega t}{2}$$

$$\therefore P = \frac{V_m I_m}{2} \sin(2\omega t)$$

This is eqⁿ for instantaneous power.


(2ω) means double the original freq. (ω)

- Average power: trying to write

$$P_{av} = \int_0^{2\pi} p$$

$$P_{av} = 0.$$


- Waveform for Power (purely inductive)

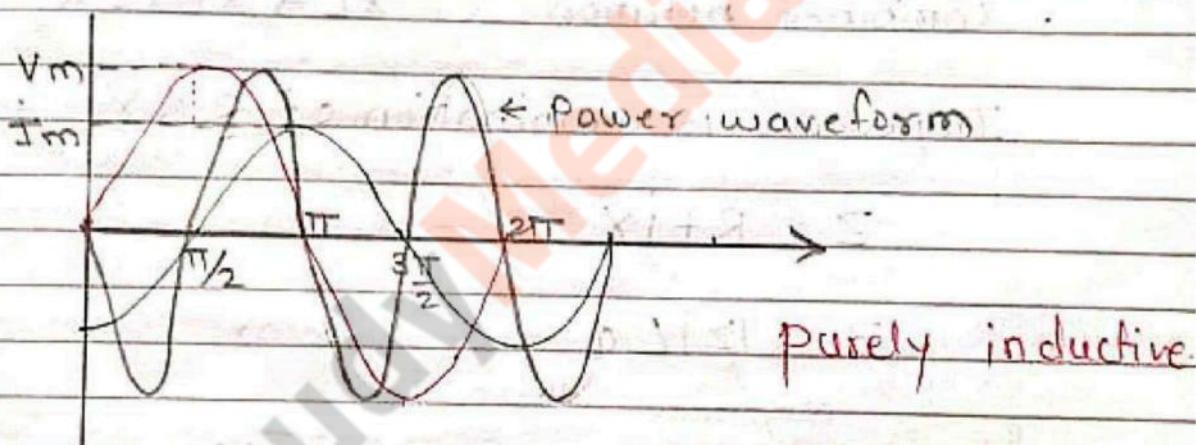

for inst. power equal zero - re cycle, result

$$P_{av} = 0.$$

- Waveform for power (capacitive)

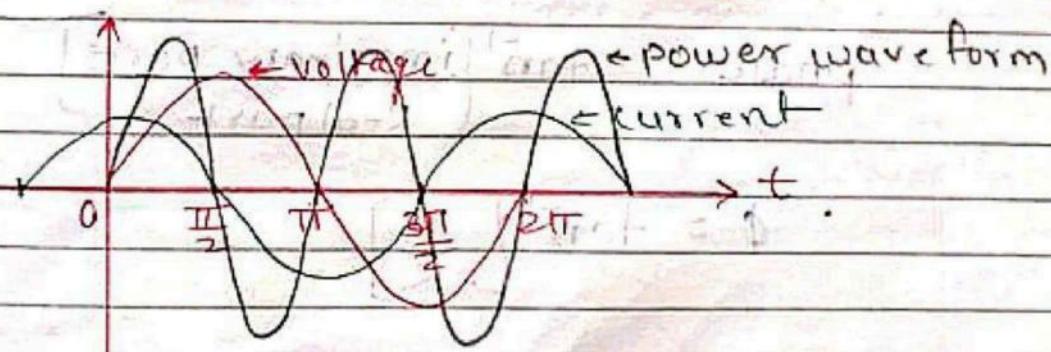

$$P_{av} = 0.$$