

JOIN **PUNE ENGINEERS** **PUNE ENGINEERS** **WHATSAPP CHANNEL**

All Subject Notes:

<https://www.studymedia.in/fe/notes>



JOIN COMMUNITY OF 30K+ ENGINEERS

CLICK HERE TO JOIN



SCAN ME



Module 1

Page No.

Elementary Concepts of DC Circuits.

Elementary concepts 4

Resistance (R):

- The opposition to the flow of current.
- Measured in ohms (Ω).
- Symbol R
- Every material (metals, semiconductors, insulators) has resistance.
- Resistance of metal is low while insulators have very high resistance.
- Metals - resistance small hence good conductors of electricity.
- Insulators - bad conductors of electricity.
e.g. plastic, wood, glass etc.

Mathematical expression for resistance -

$$R = \rho \frac{l}{a}$$

ρ = resistivity of material if it is cont.

l = length of conductor.

a = cross sectional area.

Factors affecting the resistance value -

- R depends on ρ , l and a .
- Also depends on temperature.
As temp. \uparrow , resistance \uparrow . Because length of a conductor will change which will change the value of R .

Resistivity or specific resistance (ρ) -

$$\rho = \frac{R \times a}{l}$$

$$\rho = \frac{\Omega \times m^2}{m} = \Omega \cdot m \rightarrow \text{unit}$$

• Ohm's law, factors like current density, time, voltage, etc. are not considered.

Defⁿ of ρ -

Resistivity is defined as the resistance of the piece of material which is 1 meter long & of unit cross sectional area.

i.e. $\rho = R$ if $l = 1\text{ m}$ & $a = 1\text{ m}^2$

Best conductor has the lowest value of specific resistance.

- Conductance (G)

It is defined as the reciprocal of resistance.

$$G = \frac{1}{R}$$

\therefore Unit of G is $\frac{1}{\Omega} = \text{S}^{-1}$ or Siemens.

conductivity (σ) -

- It is defined as reciprocal of the resistivity.
Its unit is $(\text{cm})^{-1}$ or Siemens/meter.

e.g. - The resistivity of copper is 1.724 micro-ohm-cm.
Find the resistance of a copper rod having dia. of 1mm & length of 1m.

$$\rightarrow R = \rho \frac{l}{a}$$

$$= 1.724 \times 10^{-6} \times \frac{\pi}{4} (0.1)^2$$

$$= 0.02195 \Omega$$

Here resistivity is given in cm units.

e.g. - Find res. of follo. copper wires.

1) 1 mm^2 cross-section, 100 m long.



Given that $\delta = 1.73 \text{ m-n-cm}$.

$$\rightarrow 1) R = \delta \frac{l}{a} = 1.73 \times 10^{-6} \times \frac{100 \times 10^2}{1 \times 10^{-2}} = 1.73 \Omega$$


$$2) R = 1.73 \times 10^{-6} \times \frac{200 \times 10^2}{25} = 0.001384 \Omega$$

- **Resistance** - ~~for transmission with 10% increase~~

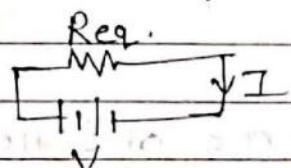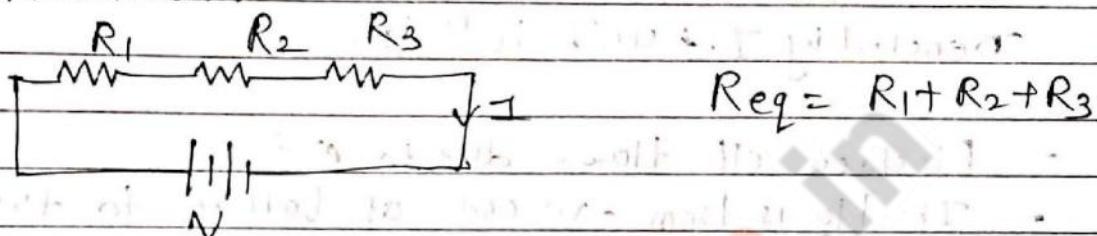Resistors in series - ~~resistance is additive~~




Resistances in parallel -

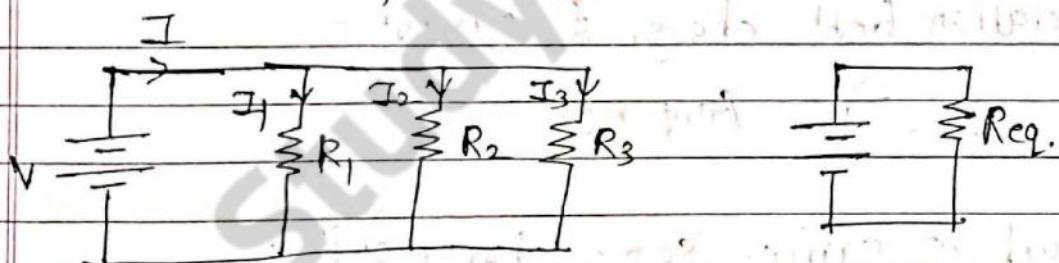

$$Req = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

- **Concept of EMF** -

EMF - Electromotive Force.

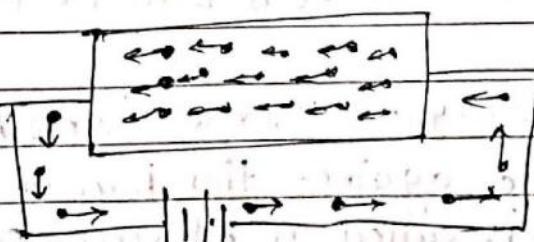

Electrical force or pressure that causes the e-s to move in a particular direction is called as EMF.

a) Unit of EMF is Volts (V).

Also called as volt or pote. diff.

Sometimes denoted by E.

- Current -

Defined as the movement of e^{-s} or flow of e^{-s} inside a conducting material.

Denoted by I. & unit is (A)

- Electron clt flows due to e^{-s}.

- It flows from -ve end of battery to +ve end.

- Conventional current -

It is said to flow from +ve end of battery to the -ve. (higher to lower potential)


- Relation b/w charge & current -

$$I = \frac{Q}{t} \text{ Amperes}$$

Each e⁻ carries some charge on it.

clt is rate of change of charge oper w.r.t. time.

- Concept of Electric potential & P.D.

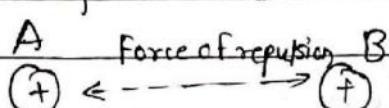

← charge B is moved to charge A.

If charge B is brought closer to charge A then work

has to be done against this force of repulsion.

- This work done is called as electric potential (V)

Potential difference (PD)

$A \bullet - \rightarrow \bullet B$

$$V_{AB} = (V_A - V_B) V.$$

The electric

The difference b/w the electric potentials at any two points is called as P.D.

It can be +ve ($V_A > V_B$)

or -ve ($V_A < V_B$)

Ohm's law

The ohm's law state that the ratio of potential diff. (V) b/w any two points and the current flowing b/w them is const. if temp is const. This ratio is termed as resistance R .

$$\frac{V}{I} = R$$

Elementary Power System

power plant generates electricity

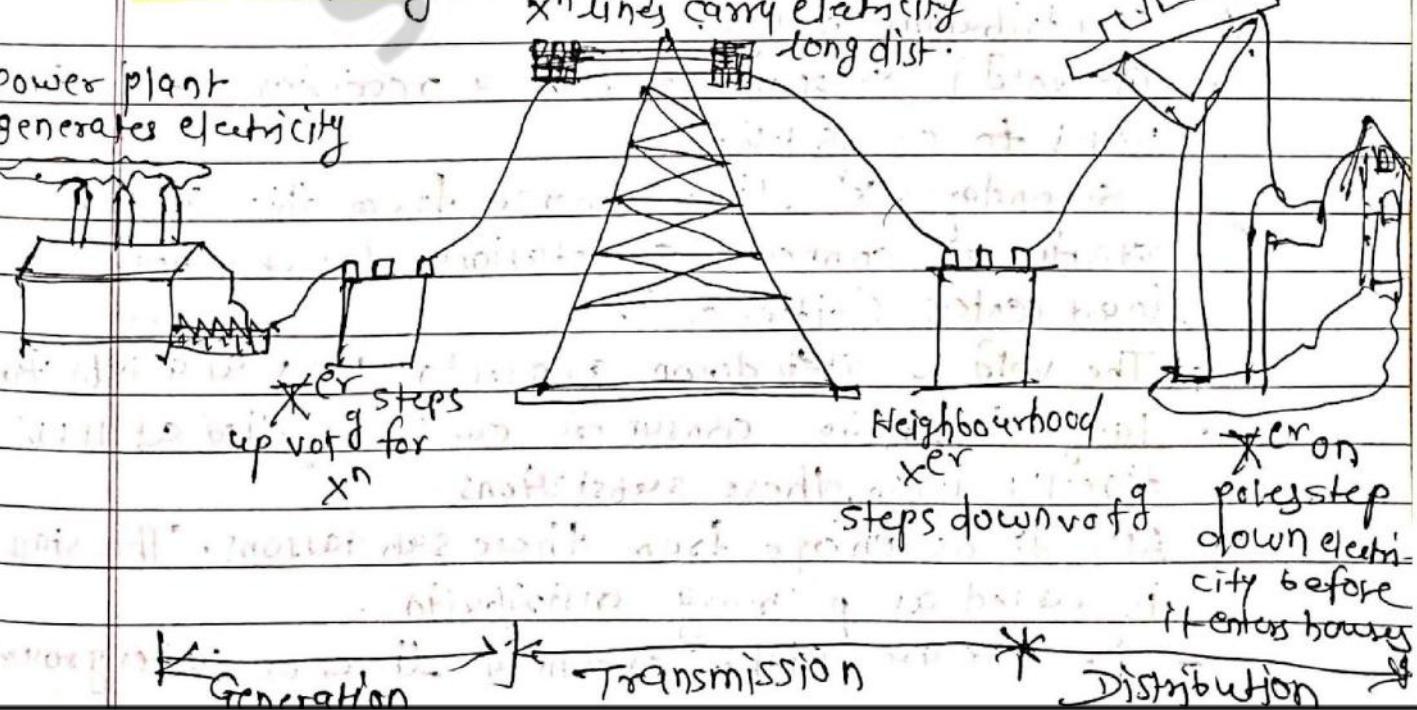


Fig. shows typical tranⁿ line that is interconnected with one another. This is known as grid.

- There are 3 stages -

① generation ② transmission ③ distribution

① Generation stage -

Power is generated at 11 KV in generating stations in India & Europe. In some cases it can be higher or lower.

② Transmission stage -

- The generating volt^g is stepped up to 132 KV,

220 KV, 400 KV or 765 KV etc.

- Stepping up volt^g depends upon the dist. at which power is to be transmitted.

- Stepping up volt^g reduces I^2R losses.

(when V is stepped up, I reduces by relative am^b so that power remains const. & hence I^2R loss also reduces.)

- This is primary tranⁿ.

③ Distribution stage -

- The volt^g is stepped down at a receiving station to 33 KV or 66 KV.

- Secondary tranⁿ lines emerge from this receiving station to connect substations located near load centers (cities etc).

- The volt^g is step down again to 11 KV at a substation.

- Large industrial consumers can be supplied at 11 KV directly from these substations.

- Also feeders emerge from these substations. This stage is called as primary distribution.

- Feeders are either overhead lines or underground

cables which carry power close to the load points (end consumers) up to a couple of km.

- Finally volt is stepped down to 415 V by a pole-mounted distribution transformer & delivered to the distributors.
- End consumers are supplied thro' a service mains line from distributors.
- Secondary distr' system consists of feeders, distributors & service mains.

Simplified block diagram of High volt AC sys-

Generating Station $\textcircled{\text{A}}$

11/132 KV Step up tr (132 KV / 220 KV / 400 KV)

Primary transmission

132 KV Step down tr (132 / 33 KV)


Receiving station



Secondary transmission

33 KV Step down tr (33 KV / 11 KV)

Substation

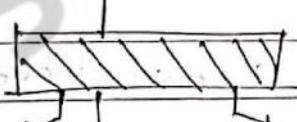

Primary distribution

11 KV Distribution tr (11 KV / 415 V)

Secondary distribution

Consumers connections

Basic HVAC system

DC circuits:

Network -

A network or ckt. is an electrical conf' which electrically connects various components such as resistors, capacitors, inductors etc & vobj or clt source to each other.

Class' of electric nw. —

Active — consists of energy source. It can be vobj or clt source.

Passive — doesn't contain any energy source.

Bilateral nw — whose char. or response doesn't depend on diren of clt thro' elements in it.

e.g. resistive nw.

Unilateral —

char. response of nw depends on diren of clt thro' its elements in it then the nw is called as a unilateral nw.

Nw containing elements such as diodes, Ters etc.

Distributed nw —

If the nw elements such as resistances, capacitances, inductances are not physically separable then it is called as a distributed nw.

Lumped nw — If nw elements can be separated physically from each other, then they are called as lumped nw.

Linear n/w -

If characteristics, parameters such as R, L, C etc.

remains constant irrespective of changes in ckt, voltage
then the ckt or n/w is called as linear n/w.

Non-linear n/w. -


Parameters change their values with change in
voltage, ckt etc.

Circuit Simplification techniques -


- 1) Series-parallel combination
- 2) Use redundant branch removal
- 3) Star delta.

Series-parallel -


Practical application of series conn? -

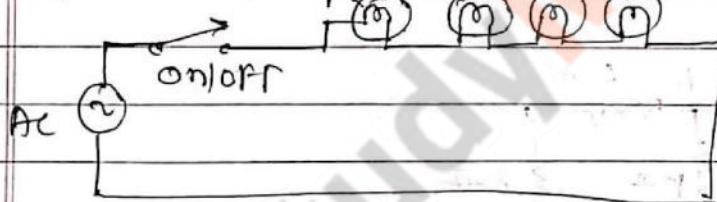






Parallel conn' -

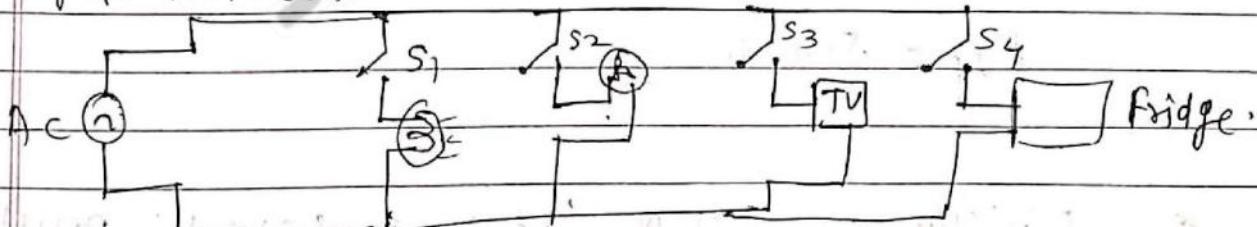

Ex: Simplify the ckt.

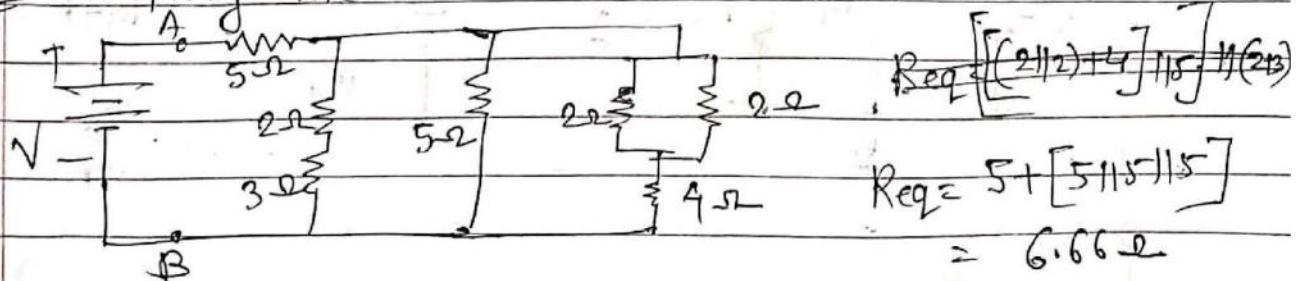


Ex

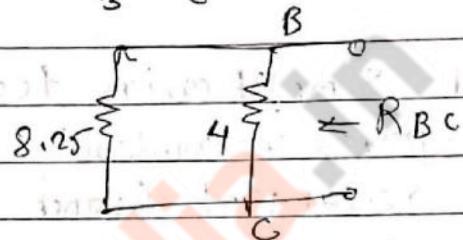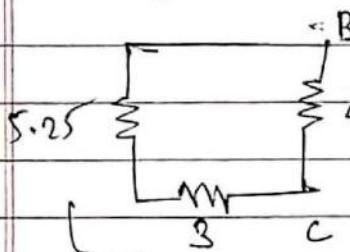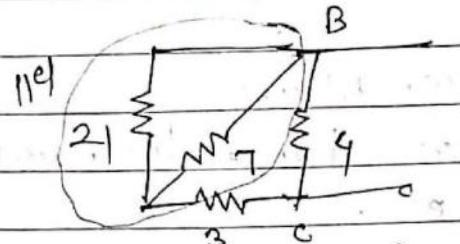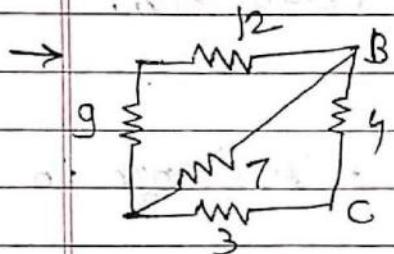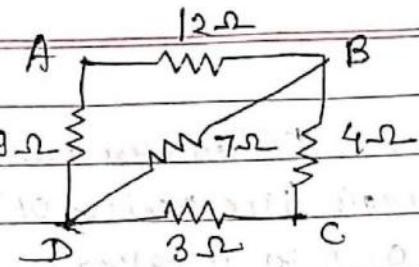Find R_{BC} -

series


$$\therefore R_{BC} = 8.25 \parallel 4$$

$$\therefore R_{BC} = 2.7 \Omega$$

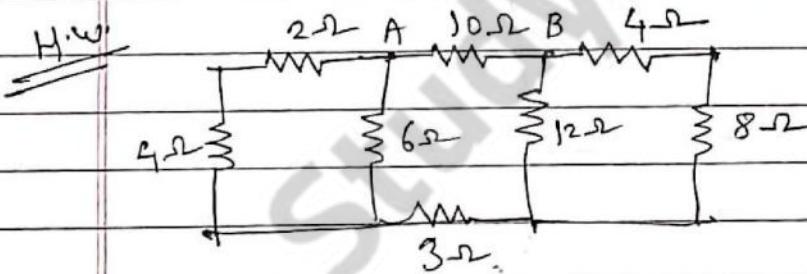


$$R_{AB} = 5.45 \Omega$$

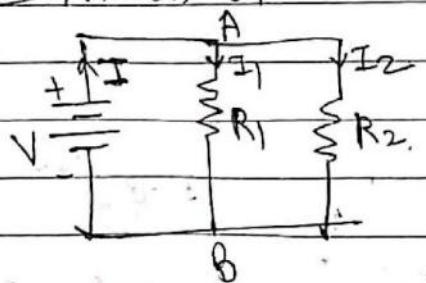* Division of current between parallel resistors -



$$I_1 = \frac{R_2}{R_1 + R_2} \times I$$

$$I_2 = \frac{R_1}{R_1 + R_2} \times I$$

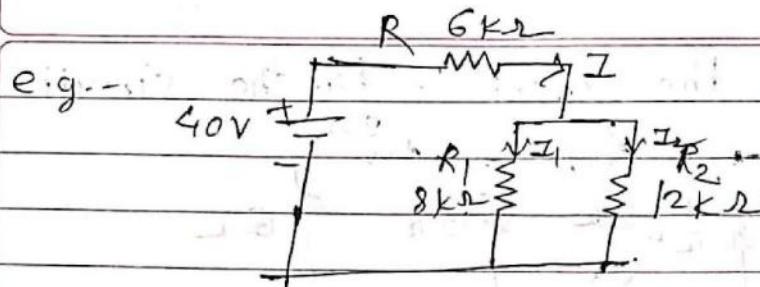

$$\rightarrow I_1 = \frac{12k}{8k+12k} \times I ; I = \frac{V}{R_{\text{Req}}} = \frac{V}{(R_1||R_2)+R}$$


$$= \frac{12k}{8k+12k} \times 3.7 \text{ mA.} \quad = \frac{40 \text{ V}}{10.8 \text{ k}\Omega} = 3.7 \text{ mA.}$$

$$= 2.22 \text{ mA.}$$


$$I_2 = I - I_1$$

$$I_2 = 3.7 - 2.22 = 1.48 \text{ mA}$$

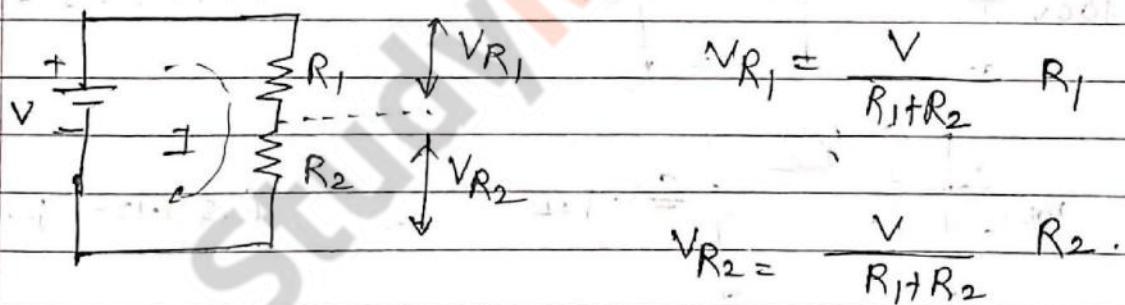* Division of voltage in the series resistors -



* Relative potential -






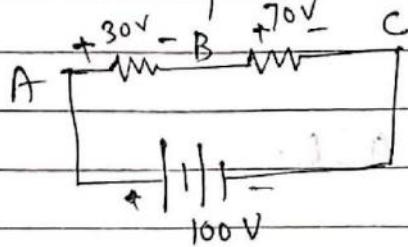


$$V_{AC} = 30 + 70 = 100 \text{ V}$$


$$V_{BC} = 70 - 30 = 40 \text{ V}$$

$$V_{AB} = 70 - 30 = 40 \text{ V}$$


$$V_{CC} = 0 \text{ V}$$

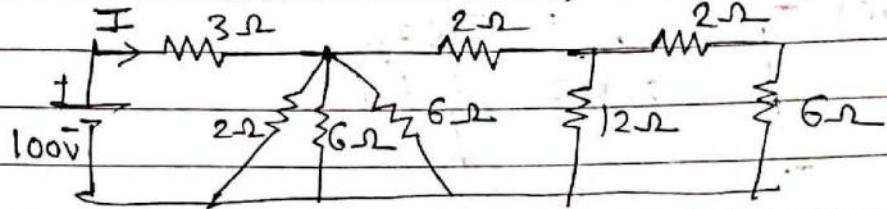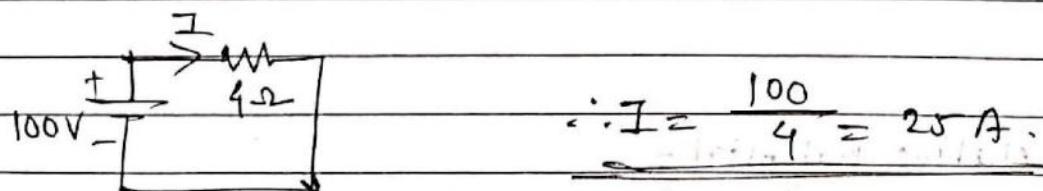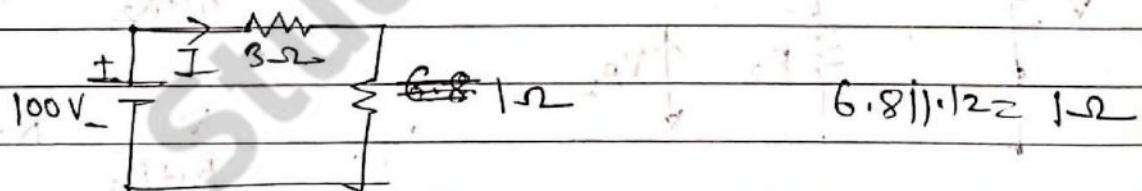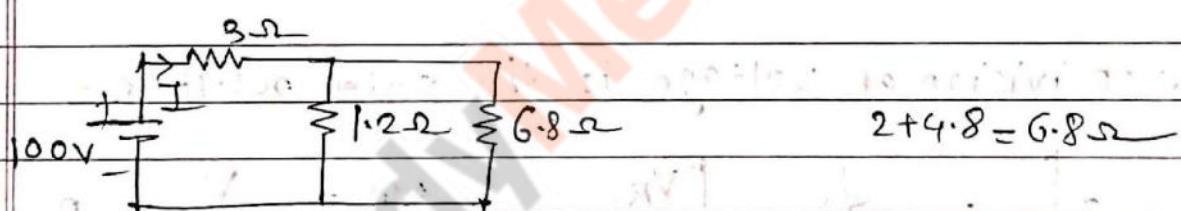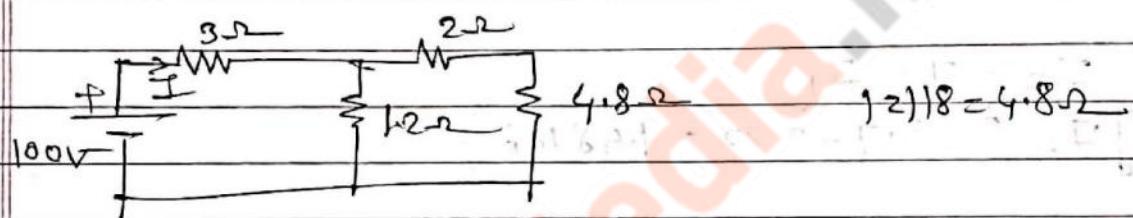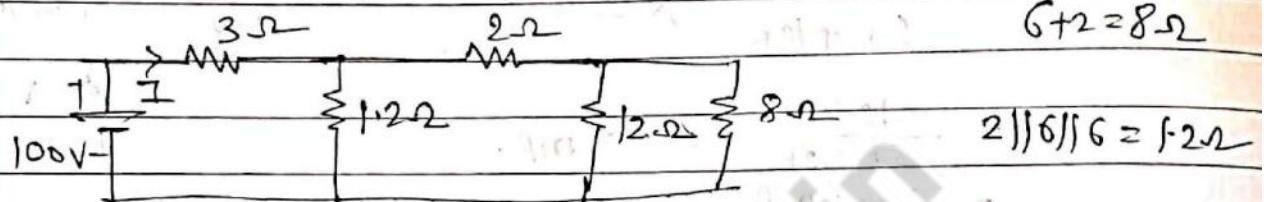ExDetermine the current I for the circuit. \rightarrow Ex


Find eq't resi. betn points A & B.

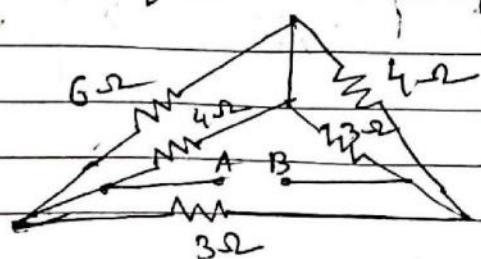
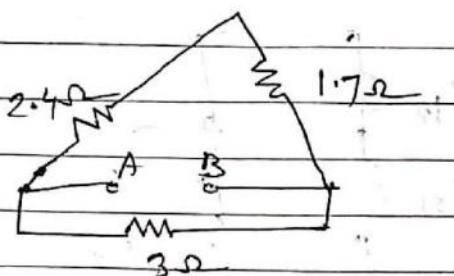
$$\rightarrow G \parallel 1 \parallel 4 \parallel 2 \quad \& \quad 4 \parallel 3 = 1.7 \parallel 2$$



$$2.4 + 1.7 = 4.1 \parallel 2$$


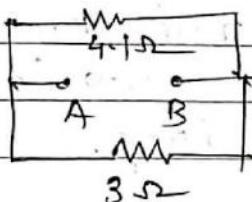


$$4.1 \parallel 3 \parallel 2 = R_{A-B}$$

$$\therefore R_{AB} = 1.732 \Omega$$

* ~~Star~~


HW. Find R_{AD}

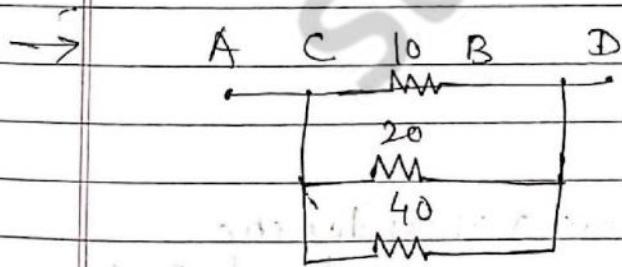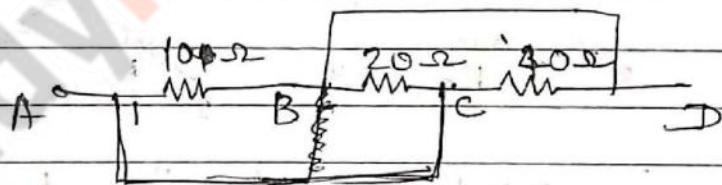


$$R_{AD} = 5.71 \Omega$$

* ~~Star-Delta & Delta-Star Transformation~~

The star network -

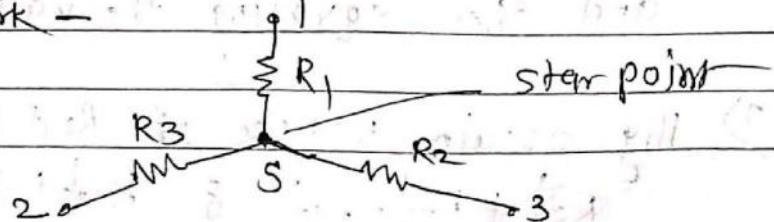


The Delta network -

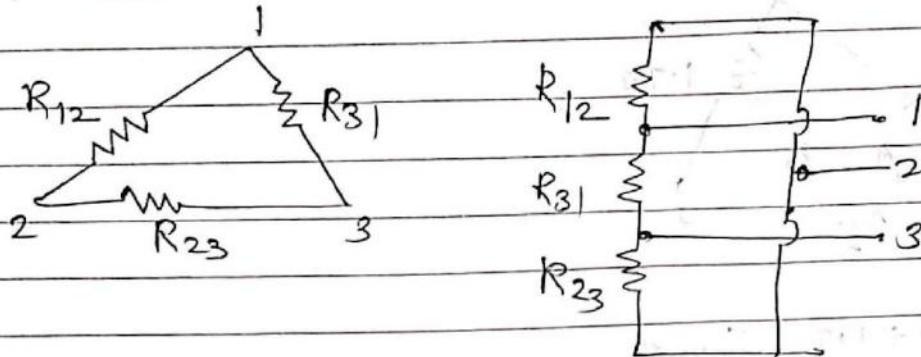

- Delta network also known as mesh connection.
- It resembles with greek letter delta (Δ)
- Three resistors form a closed loop.




* Delta to star conversion -

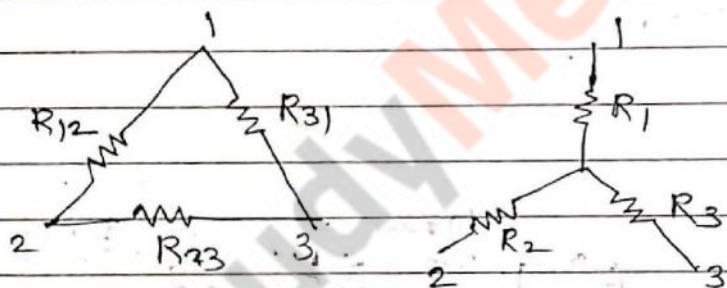

We need expression for R_1 , R_2 , R_3 in terms of R_{12} , R_{23} , R_{31} .

Steps -

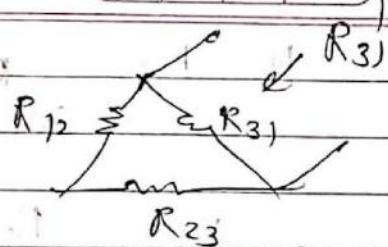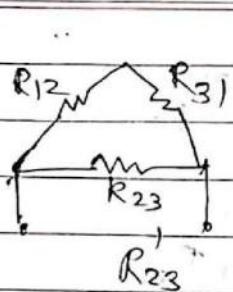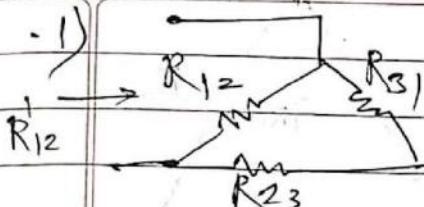- 1) Write down the resistance values for the delta and star networks. e.g. - R_{12}' , R_{23}' , R_{31}'
- 2) Obtain the value of R_1 by solving the expression $R_{12}' + R_{31}' - R_{23}'$ for star and delta networks and then equating the values for both the nets.
- 3) Similarly, obtain values of R_2 & R_3 by solving eqns $R_{31}' + R_{23}' - R_{12}'$ & $R_{12}' + R_{23}' - R_{31}'$



$$\therefore R_{12}^1 = R_{12} \parallel (R_{31} + R_{23})$$

$$R_{12}^1 = \frac{R_{12} [R_{31} + R_{23}]}{R_{12} + R_{23} + R_{31}}$$


$$R_{23}^1 = R_{23} (R_{12} + R_{31})$$

$$R_{23}^1 = \frac{R_{23} (R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

$$R_{31}^1 = R_{31} (R_{12} + R_{23})$$

$$R_{31}^1 = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}}$$

Now, for star network -

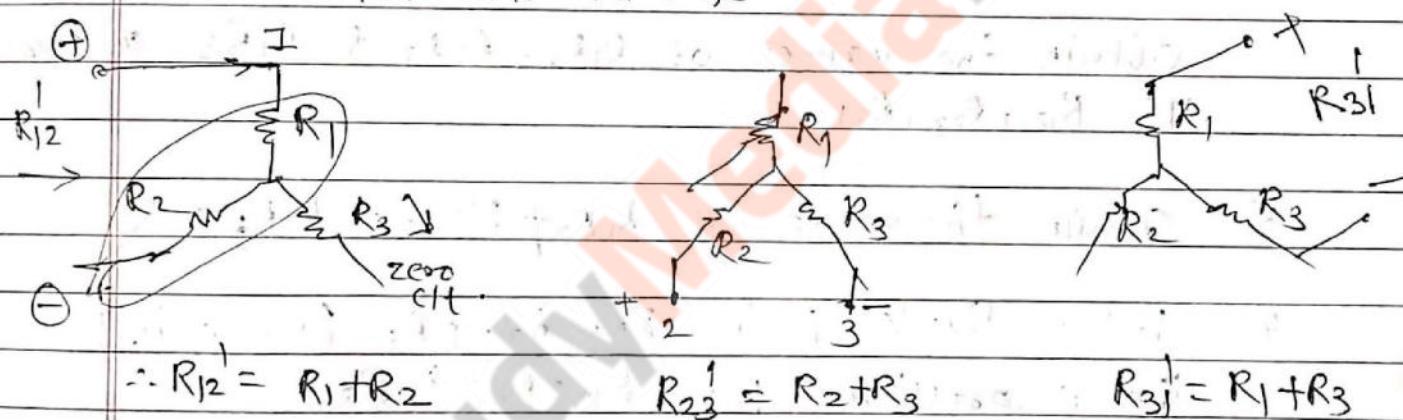

To obtain the value of R_1 -

Solve

$$R_{12}^1 + R_{31}^1 - R_{23}^1$$

$$\therefore (R_1 + R_2) + (R_3 + R_1) - (R_2 + R_3) = 2R_1 \quad \text{--- for star network}$$

$$\therefore \frac{R_{12}(R_{31} + R_{23})}{R_{12} + R_{23} + R_{31}} + \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} - \frac{R_{23}(R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}}$$


$$= \frac{2R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

--- For Delta network

$$\therefore 2R_1 = \frac{2R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \therefore R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\text{Hence, } R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}}$$
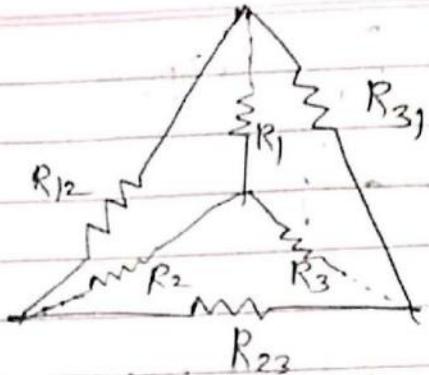
$$R_3 = \frac{R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$



* Start to Delta conversion -

- 1) Consider the resistance values between different nodes for star and delta networks
- 2) Obtain the values of R_1R_2 , R_2R_3 & R_1R_3 in terms of R_{12} , R_{23} , R_{31}
- 3) Obtain the values of $R_1R_2 + R_2R_3 + R_1R_3 = R$
- 4) Now divide R by R_1 , R_2 & R_3 to obtain the expressions for R_{12} , R_{23} & R_{31}

II) We know,

$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

Now find

$$R_1 R_2 = \frac{R_{12}^2 R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})^2}$$

$$R_2 R_3 = \frac{R_{23}^2 R_{12} R_{31}}{(R_{12} + R_{23} + R_{31})^2}$$

$$R_1 R_3 = \frac{R_{31}^2 R_{12} R_{23}}{(R_{12} + R_{23} + R_{31})^2}$$

Adding above three eqns, & dividing it by R_1 ,

$$\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1} = \frac{R_{12} R_{23} + R_{23}^2 + R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{R_{23} (R_{12} + R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$


$$\boxed{\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1} = R_{23}}$$

Divide by R_2 ,


$$\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2} = R_{31}$$

$$\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} = R_{12}$$

Ex Find the resistance betw B and C.


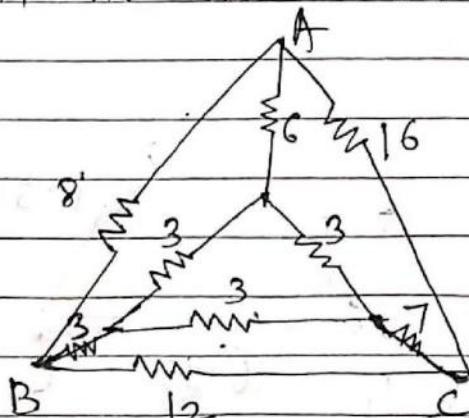


→ convert inner delta to star.

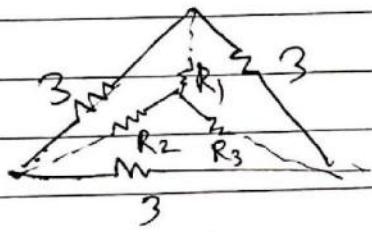


$$\therefore R_1 = \frac{3 \times 3}{3 + 3 + 3} = 1\Omega$$

$$\text{Hence } R_2 = R_3 = 1\Omega$$

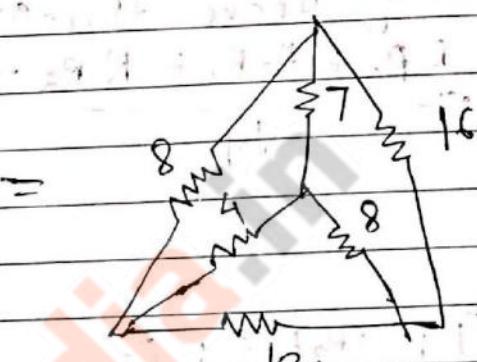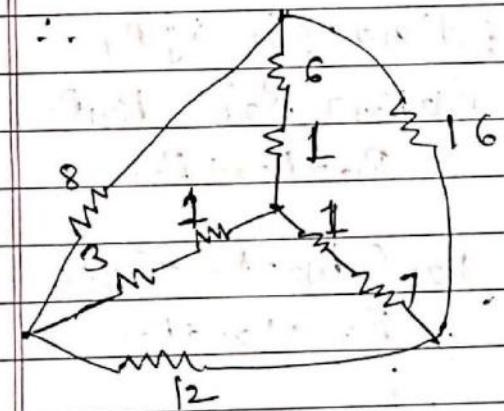

convert star to delta.
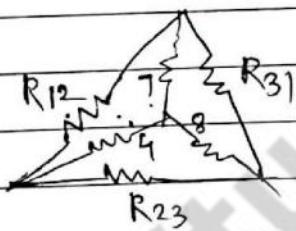
$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_2 + R_3}$$





$$R_{12} = \frac{116}{8} = 14.5\Omega$$

$$= 14.5\Omega$$


$$R_{23} = \frac{116}{7} = 16.58\Omega$$

$$R_{31} = \frac{116}{4} = 29\Omega$$

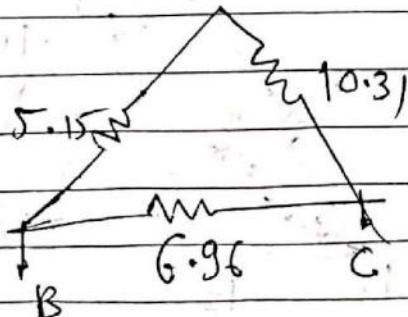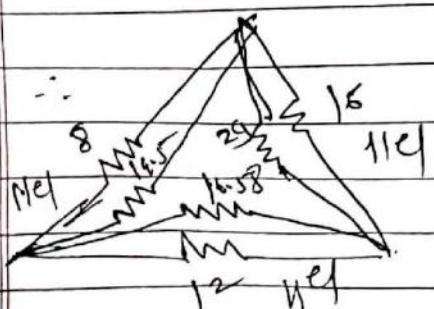


$$\therefore R_{BC} = \frac{(5.15 + 10.31) 11}{6.96} = 4.8\Omega$$

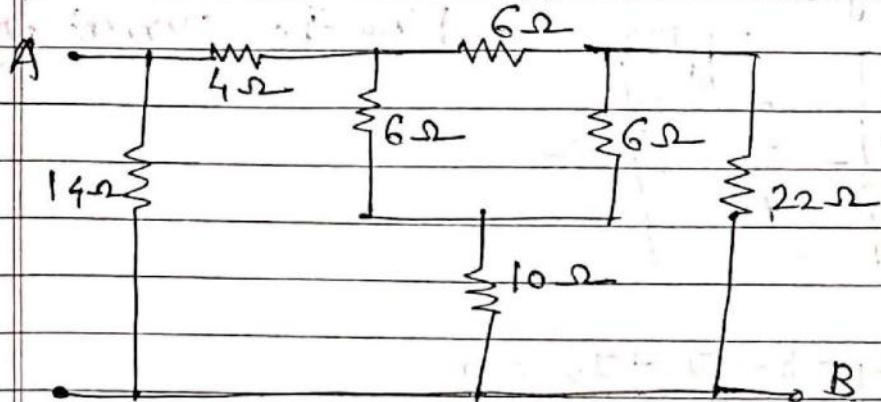H.W. Determine the effective resi. betⁿ A & B.



Ans. 7Ω

H.W. Determine eqnt resi: betⁿ xy.

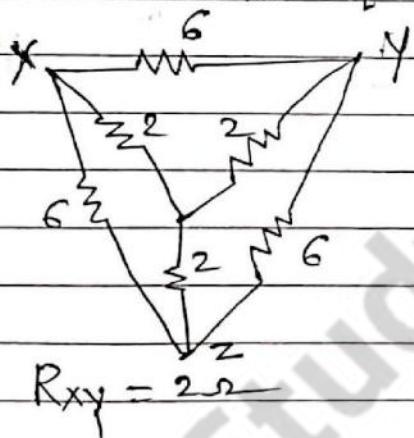

$$R_{xy} = 2\Omega$$

* Kirchhoff's Laws —


1) Current law (KCL) —

The sum of cts directed into any node in a circuit is equal to the sum of the currents coming out of same node

2) Voltage law (KVL) —

The algebraic sum of the votsⁿ around a closed loop in a circuit must be equal to zero.

* Mesh analysis -

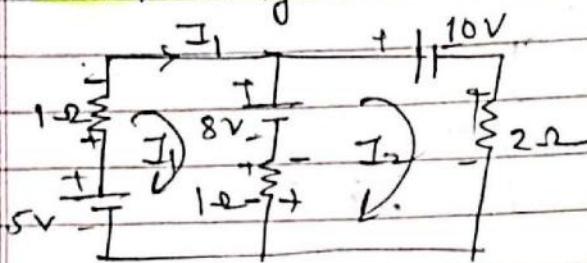

Find the current thro' 5V battery

Loop 1

$$5 - 1 \times I_1 - 8 - I_1 + I_2 = 0 \\ \therefore -2I_1 + I_2 = 3 \quad \text{--- (1)}$$


Loop 2

$$-10 - 2I_2 - I_2 + I_1 + 8 = 0 \\ \therefore -3I_2 + I_1 = 2 \\ \therefore I_1 - 3I_2 = 2 \quad \text{--- (2)}$$

$$\therefore I_1 = 2.2 \text{ A} \quad 0.8 \text{ A}$$

$$I_2 = -1.4 \text{ A}$$

H.W. Ex.

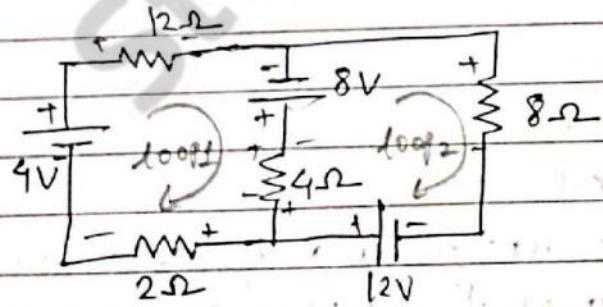

Determine all loop currents.

→ Loop 1,

$$4 - 12I_1 + 8 - 4I_1 - 2I_1 + 4I_2 = 0$$

$$\therefore 12 - 18I_1 + 4I_2 = 0$$

$$\therefore +18I_1 - 4I_2 = 12 \quad \text{--- (1)}$$

Loop 2,

$$-8I_2 + 12 - 4I_2 + 4I_1 - 8 = 0$$

$$\therefore 4 + 4I_1 - 12I_2 = 0$$


$$\therefore -4I_1 + 12I_2 = 4 \quad (2)$$

Solving (1) & (2),

$$I_1 = 0.8A$$

$$I_2 = 0.2A$$

Ex

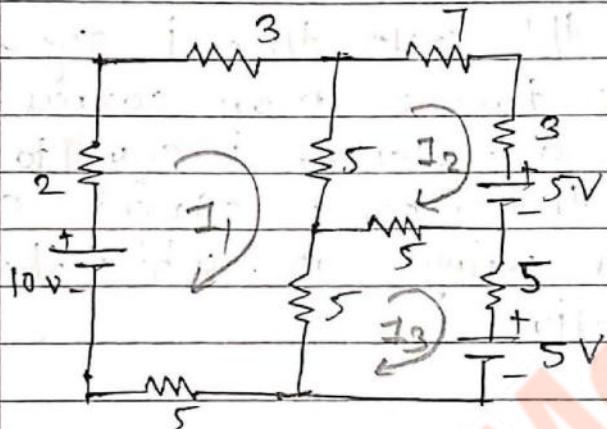

Determine all loop currents.

→ loop 1,

$$10 - 2I_1 - 3I_1 - 5I_1 + 5I_2 - 5I_1 + 5I_3 - 5I_1 = 0$$

$$-20I_1 + 5I_2 + 5I_3 = -10$$

$$\therefore 20I_1 - 5I_2 - 5I_3 = 10 \quad (1)$$

loop 2,

$$-7I_2 - 3I_2 - 5 - 5I_2 + 5I_3 - 5I_2 + 5I_1 = 0$$

$$5I_1 - 20I_2 + 5I_3 = 5 \quad (2)$$


loop 3,

$$-5I_3 - 5 - 5I_3 + 5I_1 - 5I_3 + 5I_2 = 0$$

$$5I_1 + 5I_2 - 15I_3 = 5 \quad (3)$$

Solving (1), (2), (3),
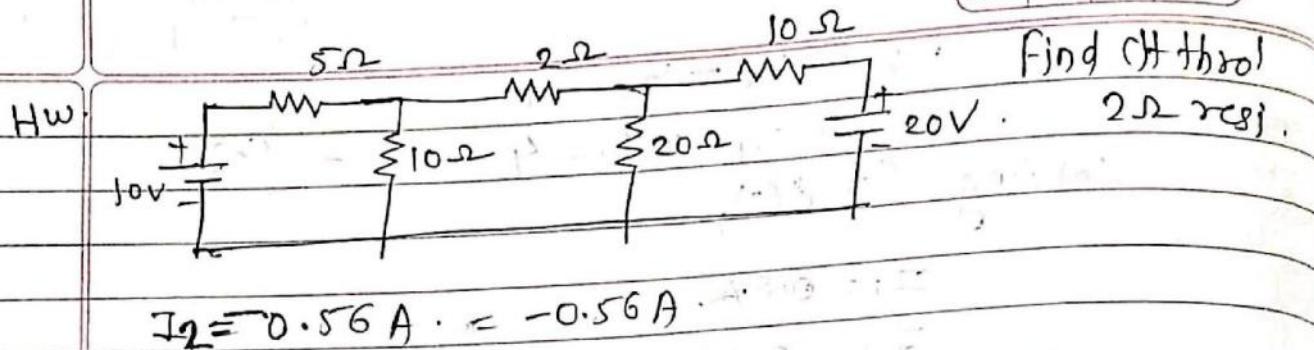
$$I_1 = 0.3714A, I_2 = -0.2285A, I_3 = -0.2857A$$



* Superposition Theorem-


The superposition thm states that in any linear network containing two or more sources, the response (current) in any element is equal to the algebraic sum of the response (current) caused by individual sources acting alone, while the other sources are inoperative.

Steps-

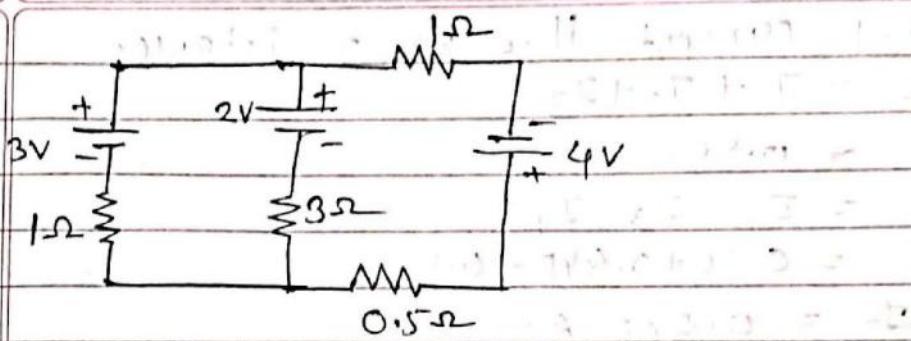- 1) Select any one energy source.
- 2) Replace all the other energy sources by:
 - Their internal series resistances for voltage sources.
 - Their internal shunt resistances for current sources.
- 3) With only one energy source calculate the voltage drops or branch currents paying attention to the voltage polarities and current directions.
- 4) Repeat steps 1, 2 and 3 for each source individually.
- 5) Add algebraically the voltage drops or branch currents obtained due to the individual source to obtain the combined effect of all the sources.


Ex-

Apply superposition thm to calculate current flowing in 3Ω resistance for the nw.



→ Step 1.

current I_1 due to 3V source.

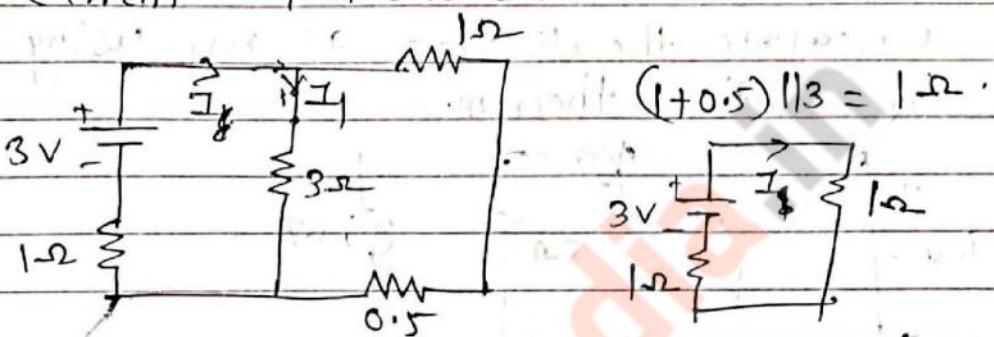


$$\therefore I_1 = \frac{3}{2} = 1.5 \text{ A}$$

$$\therefore I_1 = \frac{1.5}{4.5} = 1.5 \times \frac{1.5}{4.5} = 0.5 \text{ A} \downarrow$$

Step 2.


current I_2 due to 2V source.

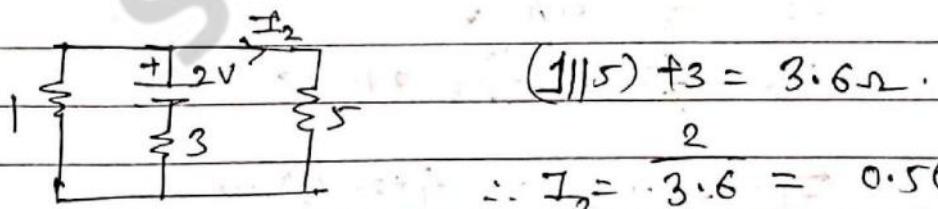

$$\therefore I_2 = \frac{2}{3.5} = 0.56 \text{ A} \uparrow$$

Step 3.

current I_3 due to only 4V source.

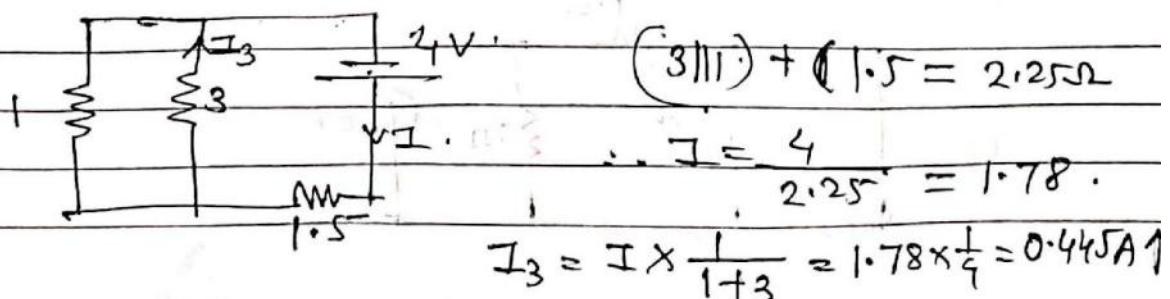

$$I_3 = I \times \frac{1}{1+3} = 1.78 \times \frac{1}{4} = 0.445 \text{ A} \uparrow$$

\therefore Total current thro' 3Ω resistance:

$$I_T = I_1 + I_2 + I_3$$


$$= 0.56$$

$$= I_2 + I_3 - I_1$$

$$= 0.56 + 0.445 - 0.5$$


$$\underline{I_T = 0.505 \text{ A}}$$

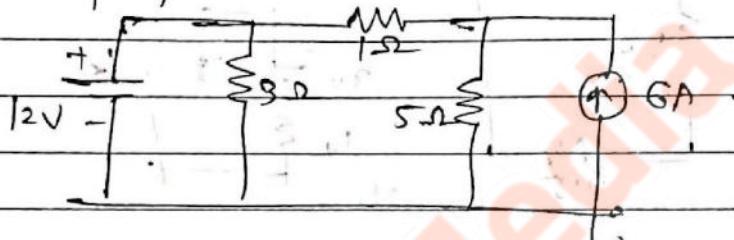Ex calculate the ckt thro' all resi. using superposition theorem.



→ Step 1:

Find ckt due to only 12V source.

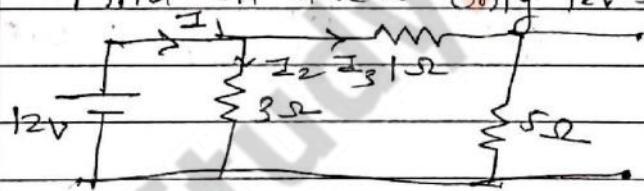


$$I_2 = \frac{12}{3} = 4 \text{ A}$$

$$I_3 = \frac{12}{5+1} = \frac{12}{6} = 2 \text{ A}$$


$$I_1 = I_2 + I_3 = 4 + 2 = 6 \text{ A}$$

Step 2:

Find current due to ckt source.

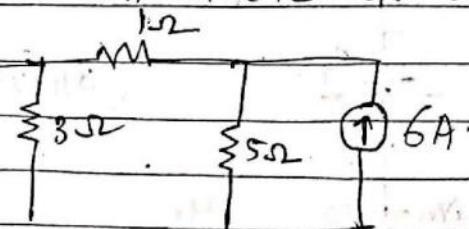

3Ω is redundant

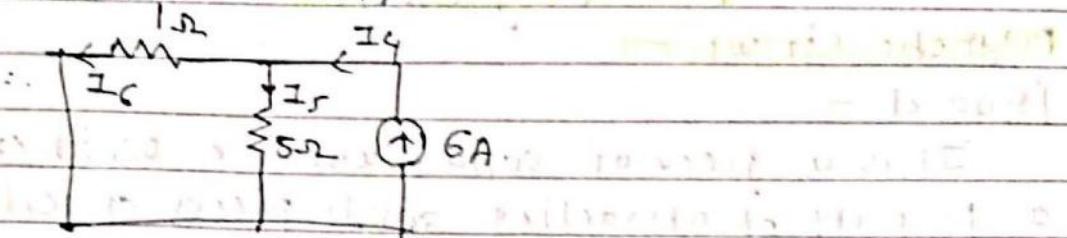

$$I_4 = 6A \uparrow$$

$$I_5 = \frac{1}{1+5} I_4 = \frac{1}{6} \times 6 = 1A \downarrow$$

$$I_6 = \frac{5}{1+5} \times 6 = 5A \leftarrow$$

-Step 3

Ckt thro' all branches -

$$1) \text{ ckt thro' } 12V \text{ source} = I_1 - I_6 = 6 - 5 = 1A \rightarrow$$


$$2) \text{ ckt thro' } 3\Omega = I_2 = 4A \downarrow$$

$$3) \text{ ckt thro' } 1\Omega = I_3 - I_6 = 2 - 5 = -3A \rightarrow = 3A \leftarrow$$

$$4) \text{ ckt thro' } 5\Omega = I_3 + I_5 = 2 + 1 = 3A \downarrow$$

$$5) \text{ ckt thro' } 6A \text{ source} = I_4 = 6A \leftarrow$$

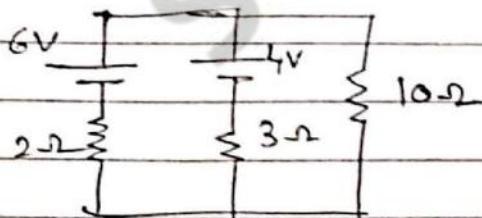Ex: Apply superposition thm to calculate ckt flowing in 10Ω resistance for the ckt.



$$I_L = 0.4637 A$$